

CS & IT ENGINEERING



CJ SIR



DIGITAL LOGIC

MINIMIZATION



Lecture No. 2



By- CHANDAN SIR

TOPICS TO BE COVERED

01 Minimization

02 Question Practice

03 Discussion

✓ SOP

✓ POS

✓ Standard Canonical
—

$$\# \quad A + B \cdot C = (A + B) \cdot (A + C)$$

$$A \cdot (B + C) = AB + AC$$

$$\# \quad AB + \bar{A}C + BC = AB + \bar{A}C$$

$$\# \quad (A + B) \cdot (\bar{A} + C) = AC + \bar{A}B$$

$$\# \quad \overline{ABC} = \bar{A} + \bar{B} + \bar{C}$$

$$\overline{\bar{A} + \bar{B} + \bar{C}} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

Q.5

P
W

Minimize the expression.

$$f(A, B) = \overline{A} \overline{B} + \overline{A} B + A \overline{B} + AB$$

$$= 1$$

$n=1$ (A)

A	{}	+
\bar{A}		
0		
1		

 $n=2$ (A, B)

$\bar{A}\bar{B}$	$\bar{A}+\bar{B}$	A	0
$\bar{A}B$	$\bar{A}+B$	\bar{A}	1
$A\bar{B}$	$A+\bar{B}$	B	$\bar{A}B+A\bar{B}$
AB	A+B	\bar{B}	$\bar{A}\bar{B}+AB$

 $\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} = 16$

n -Variable \rightarrow q^q^n distinct function.

Q.6

P
W

Minimize the expression.

$$f(A, B) = \bar{A}B + \bar{A}B$$

$$= \bar{A}B$$

$$\underline{\underline{AB}}$$

$$f(A, B) = \bar{A}B + A\bar{B} \rightarrow \text{already minimize}$$

$$= A \oplus B$$

$$f(A, B) = \bar{A}\bar{B} + AB$$

$$= A \ominus B$$

Q.7

P
W

Minimize the expression.

$$f(A, B) = AB + \bar{A} C + BC$$

~~AB + AC~~

→ function written in wrong format.

$$\begin{aligned} f(B, A) &= \bar{A} \bar{B} + \bar{A} B + A \bar{B} \\ &= \bar{B} \bar{A} + B \bar{A} + \bar{B} A \end{aligned}$$

$$f(A, C, B) = \bar{A}\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} \Rightarrow \Sigma m(0, 5, 4, 7)$$

POS of the function given below -

(A) $\Pi M(2, 5, 6)$

(B) $\Pi M(3, 4, 5, 6)$

(C) $\Pi M(0, 5, 4, 7)$

(D) None

$$\begin{aligned}
 f(A, C, B) &= \overline{\bar{A}\bar{C}\bar{B}} + AC\bar{B} + A\bar{C}\bar{B} + ACB \\
 &= \Sigma m(0, 6, 4, 7) \\
 &= \Sigma m(0, 4, 6, 7) \\
 &\quad \Pi M(1, 2, 3, 5)
 \end{aligned}$$

Q.8

P
W

Minimize the expression.

$$f(A, B, C) = \overline{A} \overline{B} + \underline{\overline{A} C} + \underline{\overline{B} \overline{C}}$$

$$= \overline{A} C + \overline{B} \overline{C}$$

Redundant = $\overline{A} \overline{B}$

Q.9

P
W

Minimize the expression.

$$f(A, B, C) = (A + B)(A + C)(\bar{B} + C)$$

$$= (A+B)(\bar{B}+C)$$

Q.10

P
W

Write the function for truth table and minimize it.

A	B	Y(0/p)
$A+B$	0	0
$A+\bar{B}$	0	1 ✓
$\bar{A}+B$	1	1
$\bar{A}+\bar{B}$	1	0

In POS.

$$Y(A,B) = (A+B+1) \cdot (A+\bar{B}+0) \cdot (\bar{A}+B+1) \cdot (\bar{A}+\bar{B}+1)$$

$$= 1 \cdot (A+\bar{B}) \cdot 1 \cdot 1$$

$$= A+\bar{B}$$

A&P

$$Y = A+\bar{B}$$

In SOP.

$$Y(A,B) = \bar{A}\bar{B} \cdot 1 + \bar{A}B \cdot 0 + A\bar{B} \cdot 1$$

$$+ AB \cdot 1$$

$$= \bar{A}\bar{B} + A\bar{B} + AB \leftarrow$$

$$\Rightarrow \bar{B}(\bar{A}+A) + AB$$

$$\Rightarrow \bar{B} + AB$$

$$= (A+\bar{B})(B+\bar{B}) = A+\bar{B}$$

A&P

Q.11

P
W

Write the function for truth table and minimize it.

A	B	Y(0/p)
0	0	C
0	1	\bar{C}
1	0	1
1	1	1

$$Y = A + Z$$

$$= A + \bar{B}C + BC$$

AnsSOP

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B} + AB$$

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A(\bar{B} + B)$$

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A$$

$$Y = \bar{A}[\bar{B}C + B\bar{C}] + A$$

$$Y = \bar{A}Z + A$$

$$Y = (\bar{A} + A) \cdot (A + Z)$$

$$\bar{B}C + B\bar{C} : Z$$

Q

$$Y = \bar{A}\bar{B}\bar{C} + \textcircled{\bar{A}\bar{B}C} + \bar{A}BC$$

$$Y = \underline{\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C} + \bar{A}BC + \bar{A}\bar{B}C$$


$$Y = \bar{A}\bar{B}(\bar{C}+C) + \bar{A}C(B+\bar{B})$$

$$Y = \bar{A}\bar{B} + \bar{A}C$$

AQ

Two way
switch

↓
 $X \oplus R$
=====

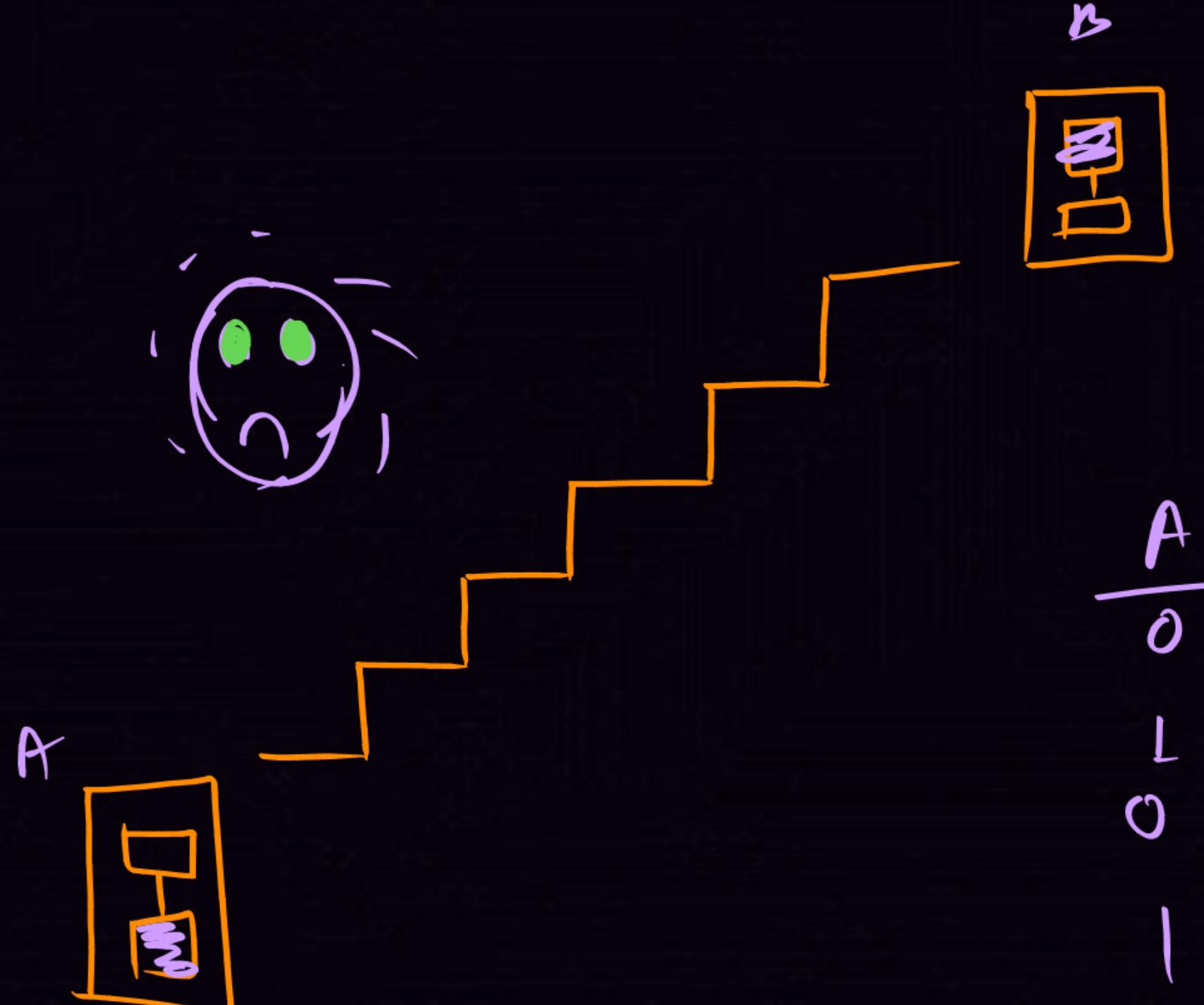

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	0

Q.13

PW

If we have '4' variable, then total different expression will be?

$$2^{2^n} \rightarrow 2^{2^4} \Rightarrow 2^{16} \Rightarrow 2^6 \cdot 2^{10}$$

$LK \rightarrow \underline{1024}$.

$$\Rightarrow 2^6 k$$
$$\Rightarrow \underline{64k}$$

$$2^4 \rightarrow 16$$

$$2^5 \rightarrow 32$$

$$2^6 \rightarrow 64$$

$$2^7 \rightarrow 128$$

$$2^8 \rightarrow 256$$

$$2^9 \rightarrow 512$$

$$2^{10} \rightarrow 1024$$

$$2^{10} = K$$

$$2^{20} = M$$

$$2^{30} = G$$

$$2^{40} = T$$

Laws of Boolean Algebra

$$\begin{cases} 1 \rightarrow -5V \\ 0 \rightarrow -10V \end{cases}$$



$$\begin{cases} 1 \rightarrow 0V \\ 0 \rightarrow 5V \end{cases}$$

$$\begin{cases} 1 \rightarrow \text{HIGH} \\ 0 \rightarrow \text{LOW} \end{cases}$$

Ex

$$\begin{cases} 1 \rightarrow 5V \\ 0 \rightarrow 0V \end{cases}$$
$$\begin{cases} 1 \rightarrow 0V \\ 0 \rightarrow -5V \end{cases}$$

$$\begin{cases} 1 \rightarrow \text{LOW} \\ 0 \rightarrow \text{HIGH} \end{cases}$$

Ex


$$\begin{cases} 1 \rightarrow 5V \\ 0 \rightarrow 10V \end{cases}$$

AND GATE

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE

A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0

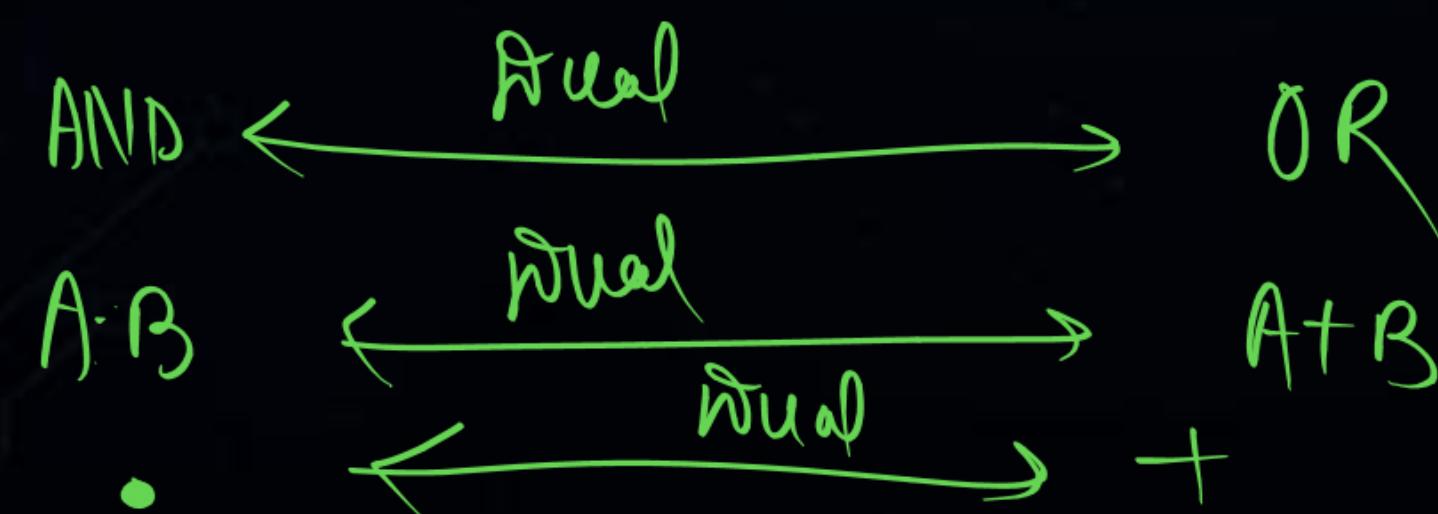

$$f = A \cdot B + C\bar{D} + \bar{E}F$$

$$f^D = (A+B) \cdot (C+\bar{D}) \cdot (\bar{E}+F)$$

$$f^D = AB + C\bar{D} + \bar{E}F$$

$$f^D = f$$


$$f = \overline{A \cdot B} \quad \text{NAND}$$

$$\xrightarrow{\text{NOR}} f^D = \overline{A + B} \quad \text{NOR}$$

Laws of Boolean Algebra

Dual

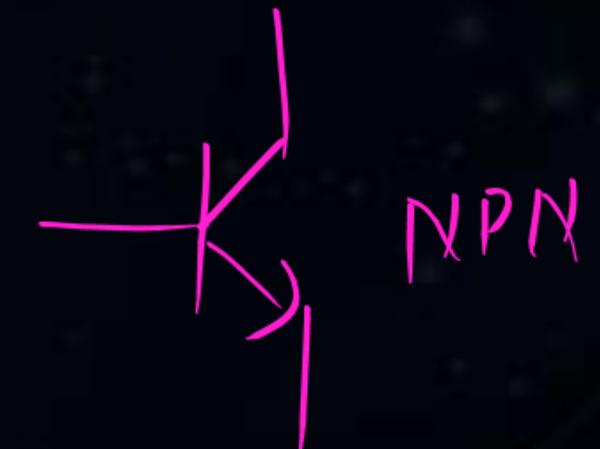
- (i) Positive logic $\xrightarrow{\text{Dual}}$ negative logic ✓
- (ii) NPN trans $\xrightarrow{\text{D}}\text{P}$ PNP trans
- (iii) N-MOS \rightarrow P-MOS
- (iv) $0 \xleftrightarrow{\text{P}} 1$
- (v) $. \xleftrightarrow{\text{P}} +$



NPN \rightarrow Transistor

PNP \rightarrow Transistor

MOS \rightarrow MOSFET.


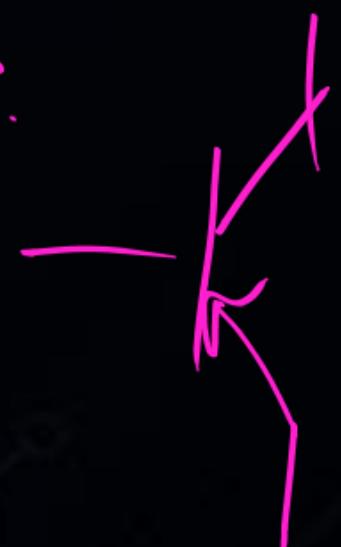


Laws of Boolean Algebra

Dual

- (i) AND \leftrightarrow OR
- (ii) NAND $\xrightarrow{\text{Dual}}$ NOR
- (iii) EX-OR $\xleftrightarrow{\text{Dual}}$ EX - NOR
- (iv) BUFFER \leftrightarrow BUFFER
- (v) INVERTER \leftrightarrow INVERTER

$$\begin{array}{ccc} A & \xleftrightarrow{\text{Dual}} & \bar{A} \\ \bar{A} & \xleftrightarrow{\text{Dual}} & \bar{\bar{A}} \end{array}$$

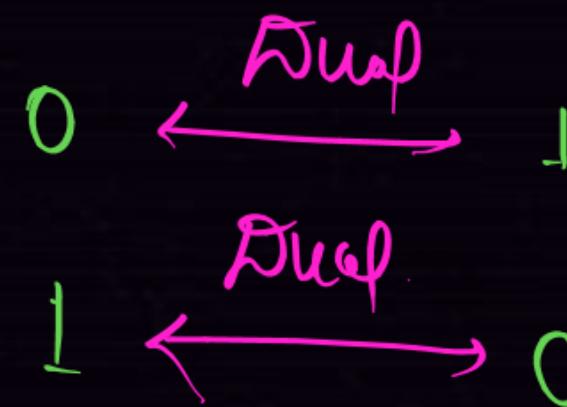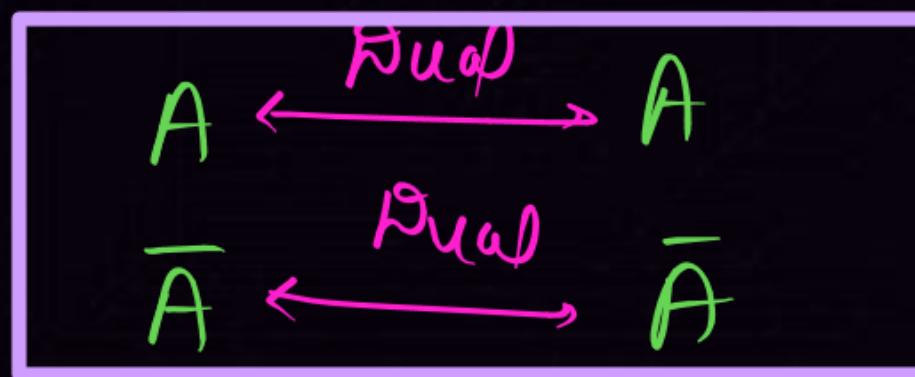
$n=1$  $n=2, (A, B)$


$$\begin{array}{ll} \bar{A}\bar{B} & \bar{A}+\bar{B} \\ \bar{A}B & \bar{A}+B \\ A\bar{B} & A+\bar{B} \\ AB & A+B \end{array}$$

A
\bar{A}
B
\bar{B}

$$\begin{array}{ll} 0 & \bar{A}B+A\bar{B} \\ 1 & \bar{A}\bar{B}+A\bar{B} \end{array}$$


$$f^P = f$$

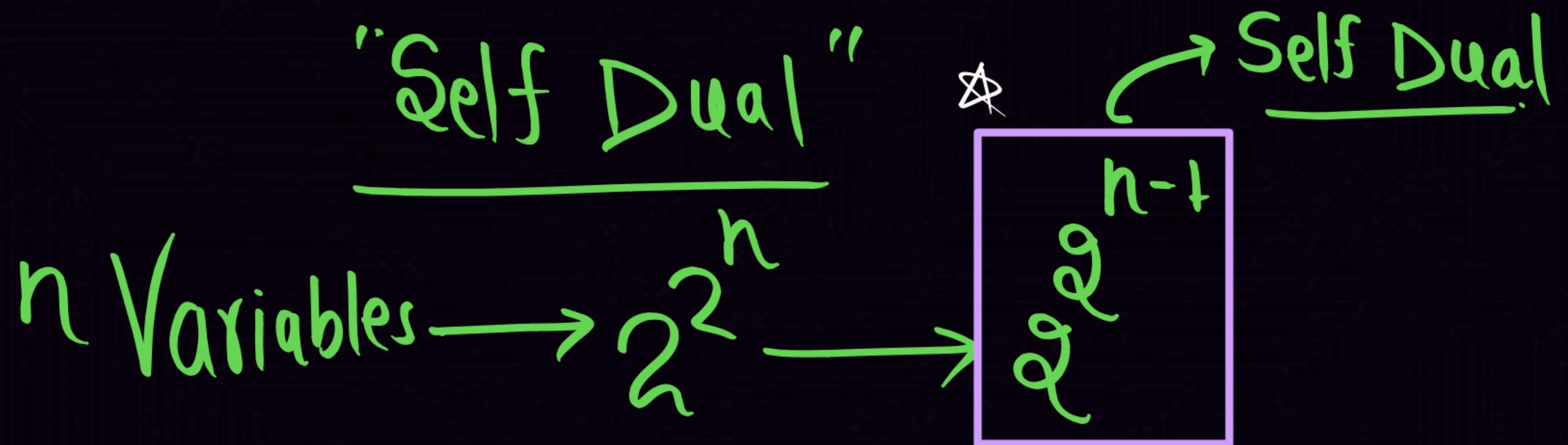

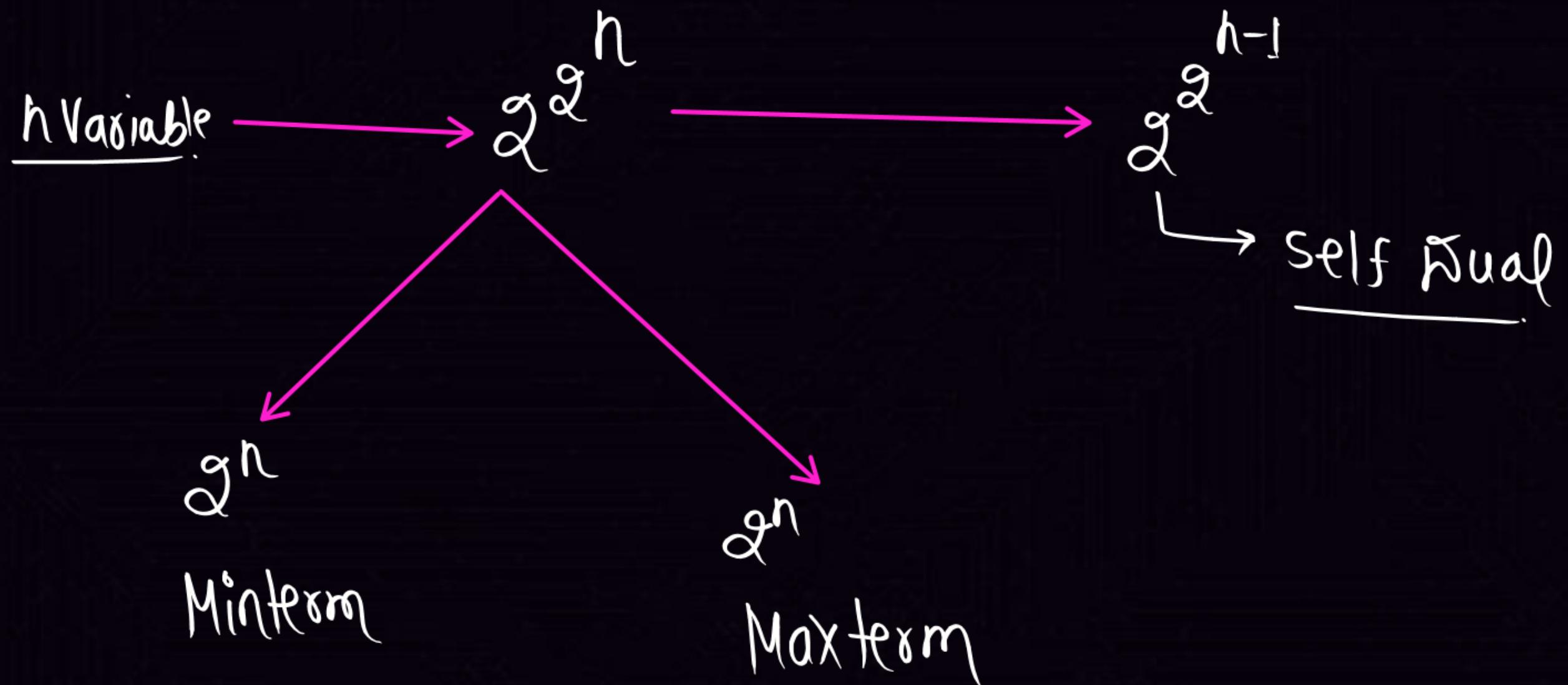

MCQ

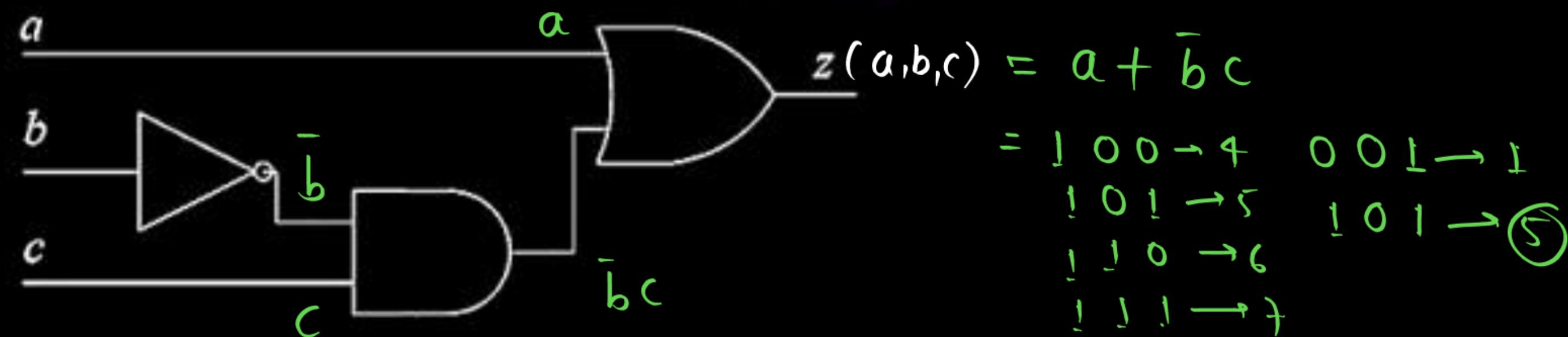Consider the Boolean function $z(a,b,c)$.



Which one of the following minterm lists represents the circuit given above?

[GATE-2020-CS: M]

- A $Z = \Sigma (0, 1, 3, 7)$
- B $Z = \Sigma (2, 4, 5, 6, 7)$
- C $Z = \Sigma (1, 4, 5, 6, 7)$
- D $Z = \Sigma (2, 3, 5)$

MCQ HW

If w, x, y, z are Boolean variables, then which one of the following is INCORRECT?

[GATE-2017-CS: M]

- A $wx + w(x+y) + x(x+y) = x + wy$
- B $\overline{w\bar{x}(y + \bar{z})} + \bar{w}x = \bar{w} + x + \bar{y}z$
- C $(w\bar{x}(y + x\bar{z}) + \bar{w}\bar{x})y = x\bar{y}$
- D $(w + y)(wxy + wyz) = wxy + wyz$

MCQ

What is the Boolean expression for the output f of the combinational logic circuit of NOR gates given below? [GATE-2010-CS: M]

A $\overline{Q+R}$

B $P+Q$

C $\overline{P+R}$

D $\overline{P+Q+R}$


$$f = (\overline{P}\overline{Q} + \overline{Q}\overline{R})(\overline{P}\overline{R} + \overline{Q}\overline{R})$$

$$f = \overline{P}\overline{Q}\overline{R} + \overline{P}\overline{Q}\overline{R} + \overline{P}\overline{Q}\overline{R} + \overline{Q}\overline{R}$$

$$f = \overline{Q}\overline{R}(\overline{P} + \overline{P} + \overline{P} + 1)$$

$$f = \overline{Q}\overline{R}$$

$$f = \overline{\overline{Q+R}}$$

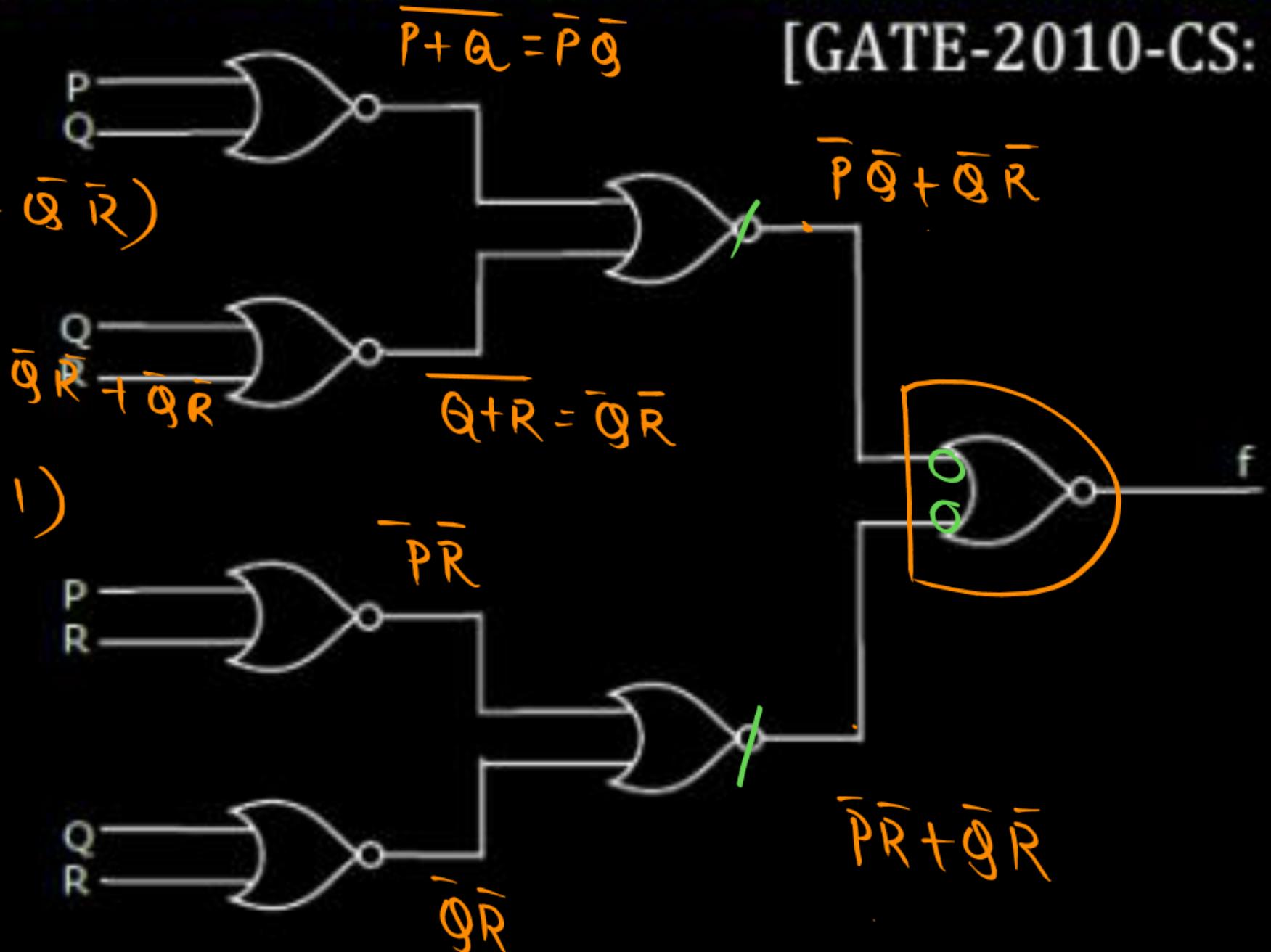

Modified Veitched Diagram

→ also known as K-MAP.

Karnaugh MAP


K-MAP

→ It is based on Gray code.

Ex


Binary → 110010

Gray → 101011

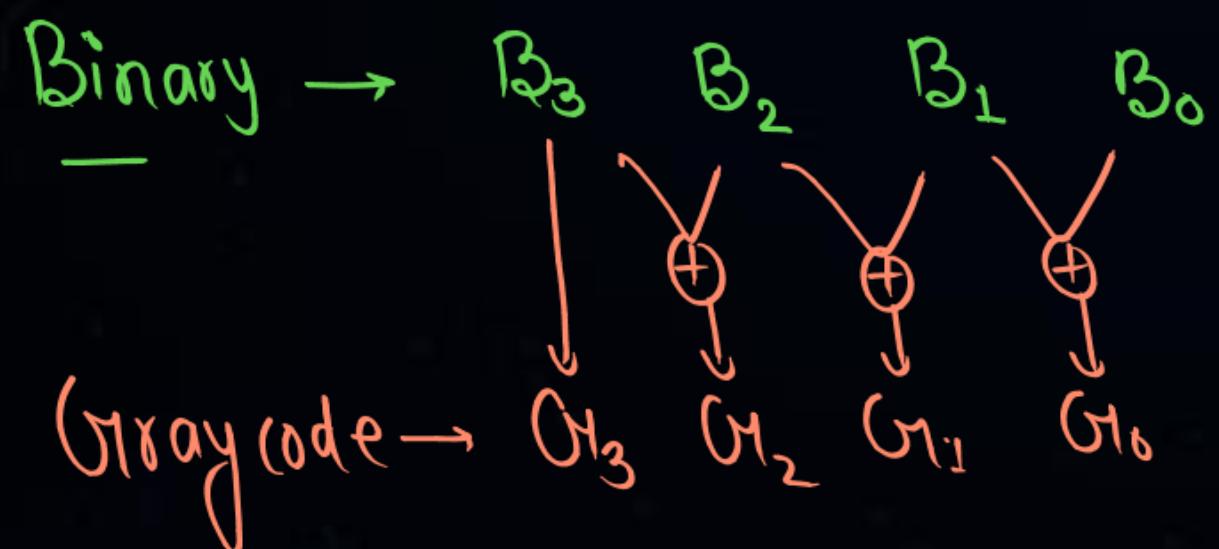

Gray code

Binary code

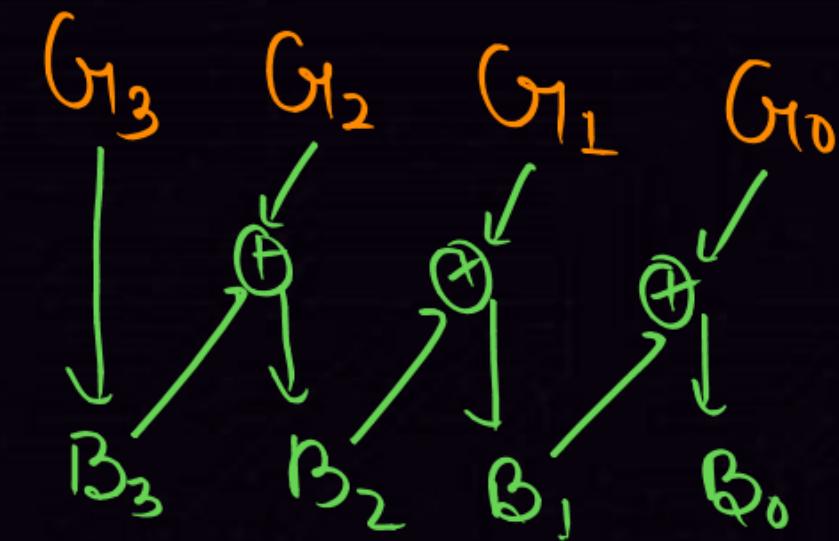

Ex Gray code \rightarrow 100101101

Binary \rightarrow 111001001 ✓

Karnaugh MAP


Decimal	Binary	Gray
0	00	00
1	01	01
2	10	11
3	11	10

Gray code.

successive numbers are differ by one bit.

- ↳ unity hamming distance code
- ↳ cyclic code
- ↳ Reflecting code.

B ≡ Q

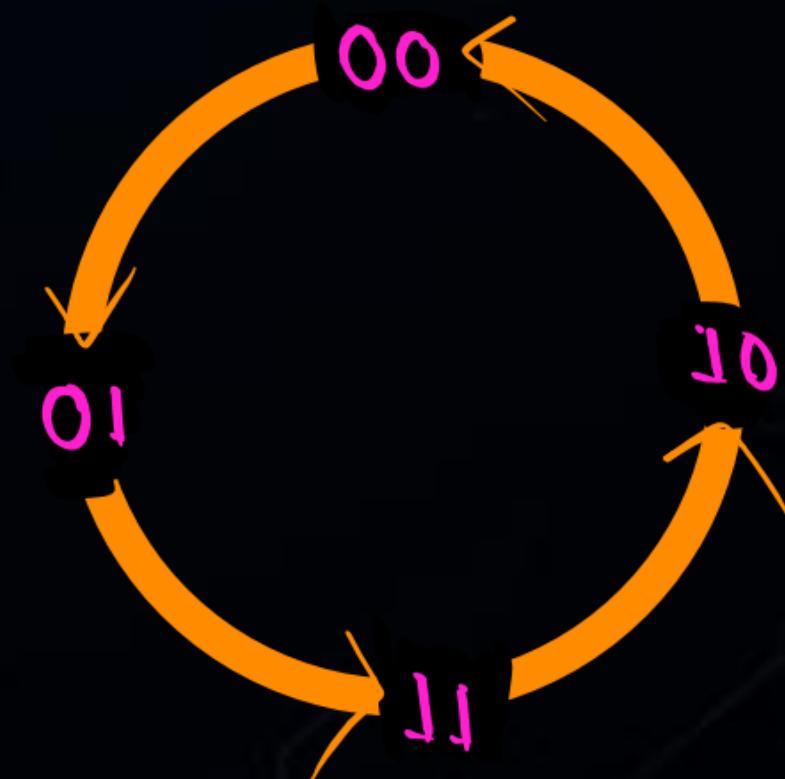

Karnaugh MAP

Decimal	Binary	Gray code
0	000	000
1	001	001
2	010	011
3	011	010
4	100	110
5	101	111
6	110	101
7	111	100

Thank you
GW
Soldiers !

