

CS & IT ENGINEERING

DIGITAL LOGIC

Combinational Circuit



Lecture No. – 01



By- CHANDAN SIR

TOPICS TO BE COVERED

01 Comparator

02 Question Practice

03 Discussion

COMPARATOR



combinational circuit

↳ A circuit without memory

↳ o/p depends only on present state of input.

Designing

✓ Comparator

✓ MUX

✓ DE-MUX

✓ Encoder

✓ Decoder

✓ HA

✓ FA

✓ H.S.

✓ F.S.

✓ Serial adder

✓ parallel adder

✓ LACA

✓ Multiplier

Designing of combinational circuit


Step 1. Find the no. of inputs and outputs.

Step 2. Write the truth table

Step 3. Write the logical expression

Step 4. Minimization

Step 5: Hardware Implementation.

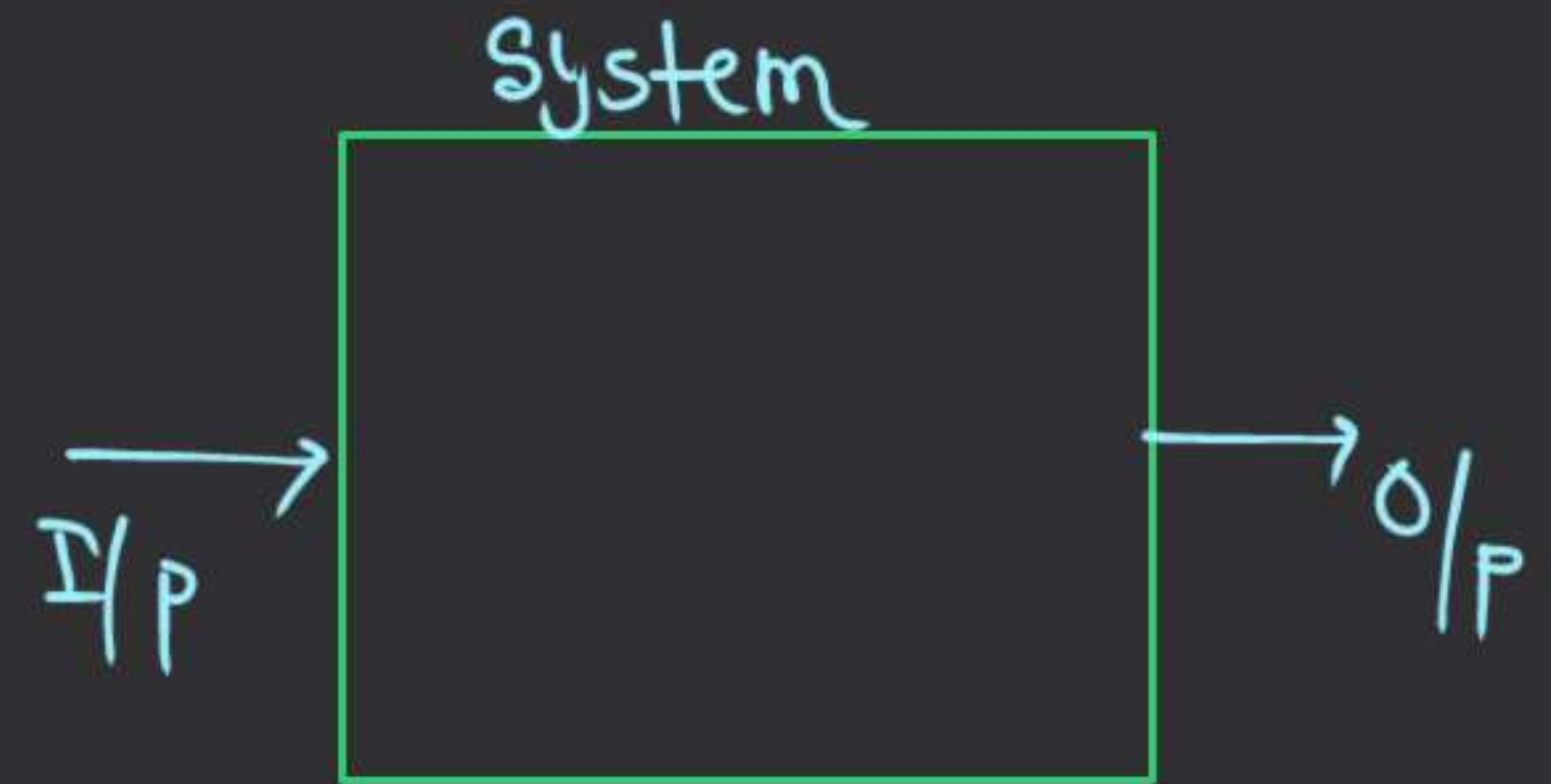


"Comparator"

Compare.

1bit
1bit

A
B

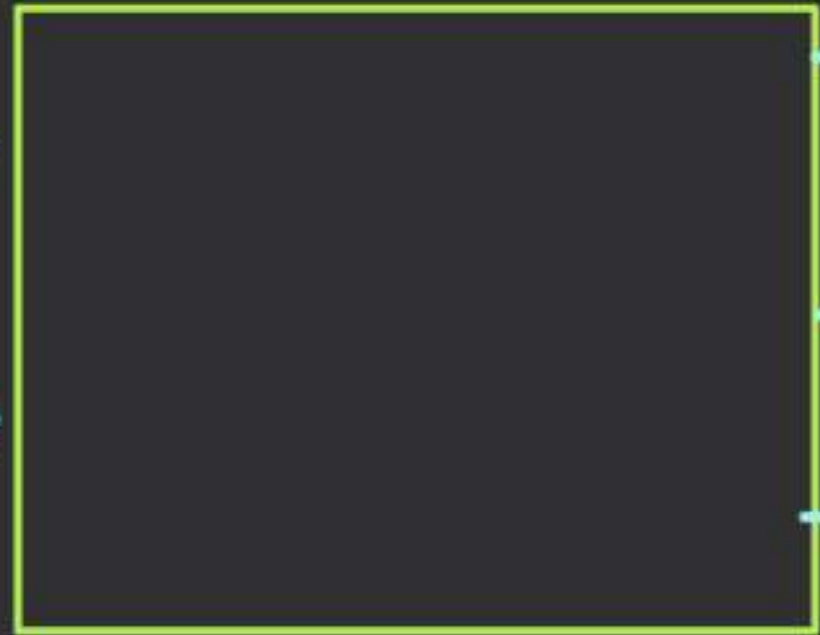

$A > B$ (x)
 $A < B$ (y)
 $A = B$ (z)

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

- Step 1. Find the number of inputs and outputs.
- Step 2. Write the truth table.
- Step 3. Write the logical expression.
- Step 4. Minimize the logical expression.
- Step 5. Hardware implementation.

COMPARATOR



DESIGNING OF COMBINATIONAL CIRCUIT

1. Design a one-bit comparator



Step 1.

Step 2. Truth Table

A	B	X (A > B)	Y (A < B)	Z (A = B)
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

COMPARATOR



DESIGNING OF COMBINATIONAL CIRCUIT

Step 3. Logical expression

$$X(A > B) = A\bar{B}$$


$$Y(A < B) = \bar{A}B$$

$$Z(A = B) = \bar{A}\bar{B} + AB = A \odot B$$

Step 4. Minimization

→ Already minimize



Step 5. Hardware implementation

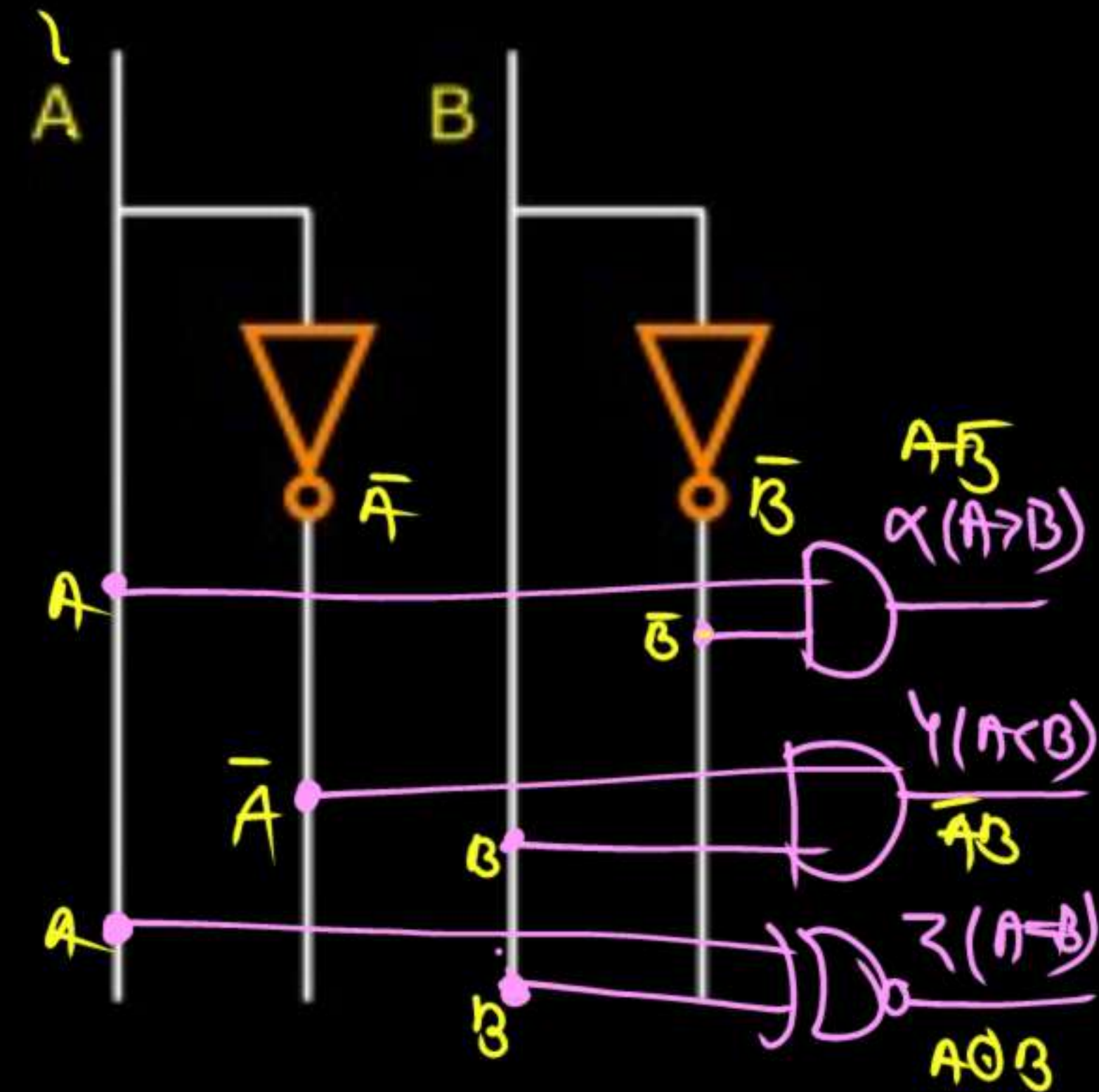

$$X(A > B) = A\bar{B}$$


$$Y(A < B) = \bar{A}B$$

$$\neg(A = B) = A \oplus B$$

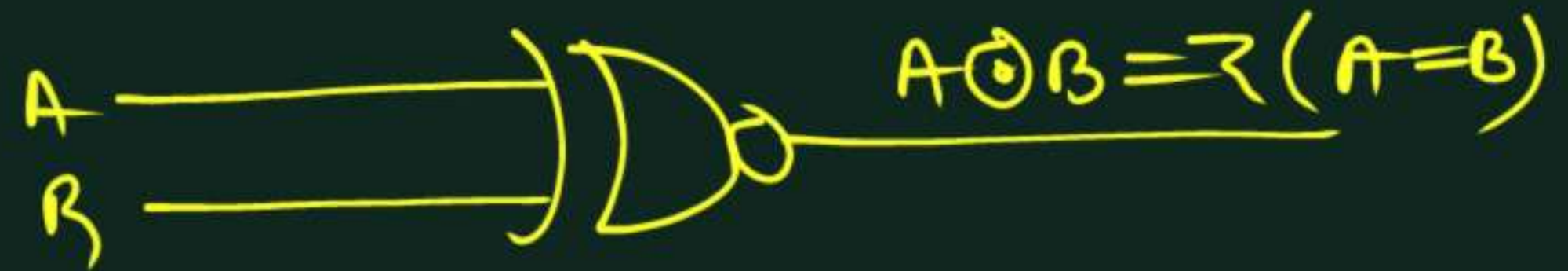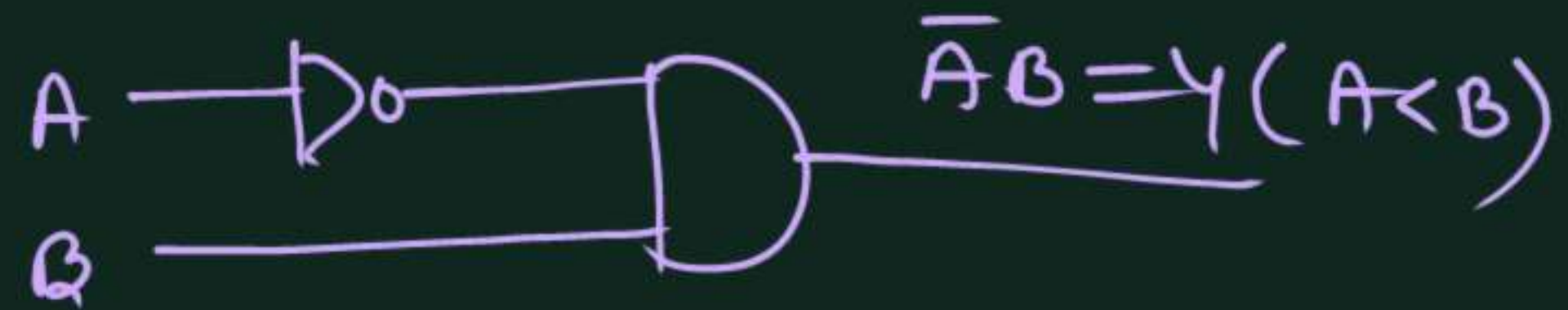

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

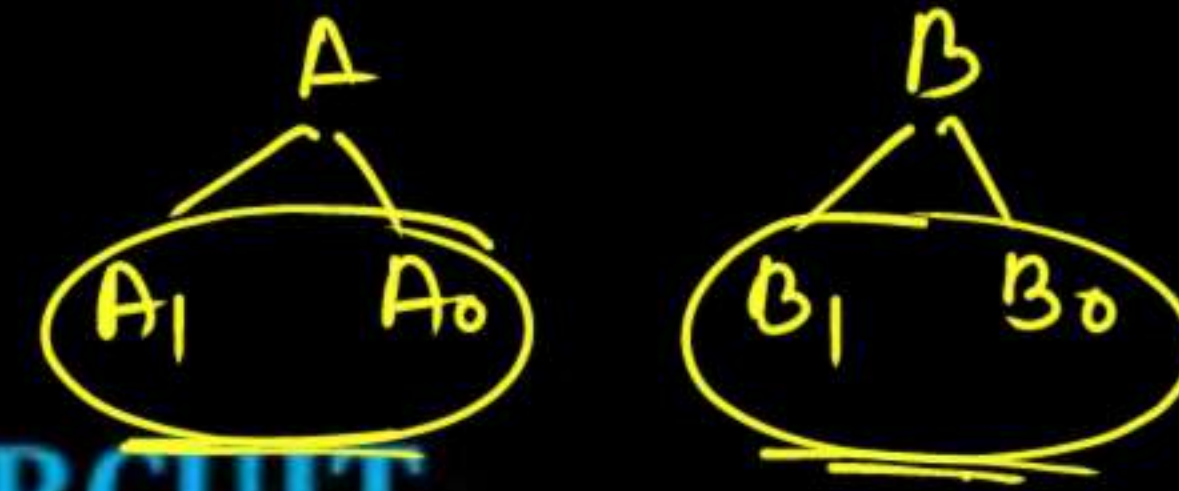

2. Design a two-Bit comparator?

Step 1.



COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 2. Truth table

	A		B		A > B	A < B	A = B
	A ₁	A ₀	B ₁	B ₀	x	y	z
0	0	0	0	0	0	0	1
1	0	0	0	1	0	1	0
2	0	0	1	0	0	1	0
3	0	0	1	1	0	1	0
4	0	1	0	0	1	0	0
5	0	1	0	1	0	0	1
6	0	1	1	0	0	1	0
7	0	1	1	1	0	1	0
8	1	0	0	0	1	0	0
9	1	0	0	1	1	0	0
10	1	0	1	0	0	0	1
11	1	0	1	1	0	1	0
12	1	1	0	0	1	0	0
13	1	1	0	1	1	0	0
14	1	1	1	0	1	0	0
15	1	1	1	1	0	0	1



COMPARATOR

$$X(A_1 A_0 B_1 B_0)$$

$$Y(A_1 A_0 B_1 B_0)$$


DESIGNING OF COMBINATIONAL CIRCUIT

Step 3. Logical expression

$$X(A > B) = \sum m(4, 8, 9, 12, 13, 14)$$

$$Y(A < B) = \sum m(1, 2, 3, 6, 7, 11)$$

$$Z(A = B) = \sum m(0, 5, 10, 15)$$

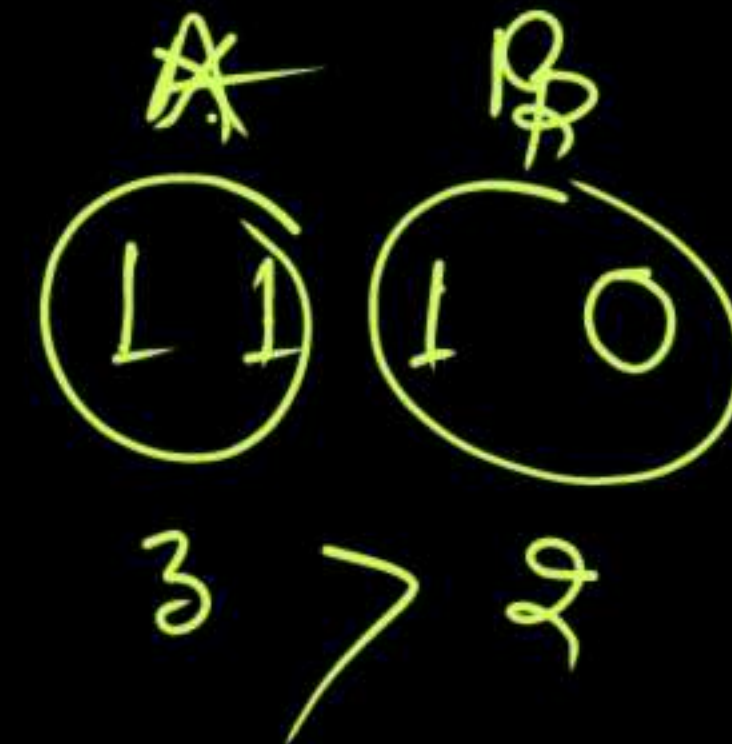

A > B

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

$$Y = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

Step 4. Minimization

For $X = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$ ✓

$A_1 A_0 \backslash B_1 B_0$		$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
		00	01	11	10
$\bar{A}_1 \bar{A}_0$	00				
$\bar{A}_1 A_0$	01				
$A_1 \bar{A}_0$	11	1	1		1
$A_1 A_0$	10	1	1		

For Y

$A_1 A_0 \backslash B_1 B_0$		00	01	11	10
$\bar{A}_1 \bar{A}_0$	00		1	1	1
$\bar{A}_1 A_0$	01			1	1
$A_1 \bar{A}_0$	11				
$A_1 A_0$	10			1	

COMPARATOR

DESIGNING OF COMBINATIONAL CIRCUIT

Step 4. Minimization

$$Z = (A_1 \odot B_1) \cdot (A_0 \odot B_0)$$

For Z

$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00	1			
01		1		
11			1	
10				1

COMPARATOR

FOR ONE BIT COMPARATOR

Total condition = 4

Equal condition = 2

Unequal condition = 2

Greater = Less condition = 1

COMPARATOR

FOR TWO BIT COMPARATOR

Total condition = 16

Equal condition = 4

Unequal condition = 12

Greater = Less condition = 6

COMPARATOR

FOR THREE BIT COMPARATOR

Total condition = 64

Equal condition = 8

Unequal condition = 56

Greater = Less condition = 281

COMPARATOR

'N' BIT COMPARATOR

Total condition = 2^{2n}


Equal condition = 2^n

Unequal condition = $2^{2n} - 2^n$

Greater = Less condition = $(2^{2n} - 2^n)/2$

COMPARATOR

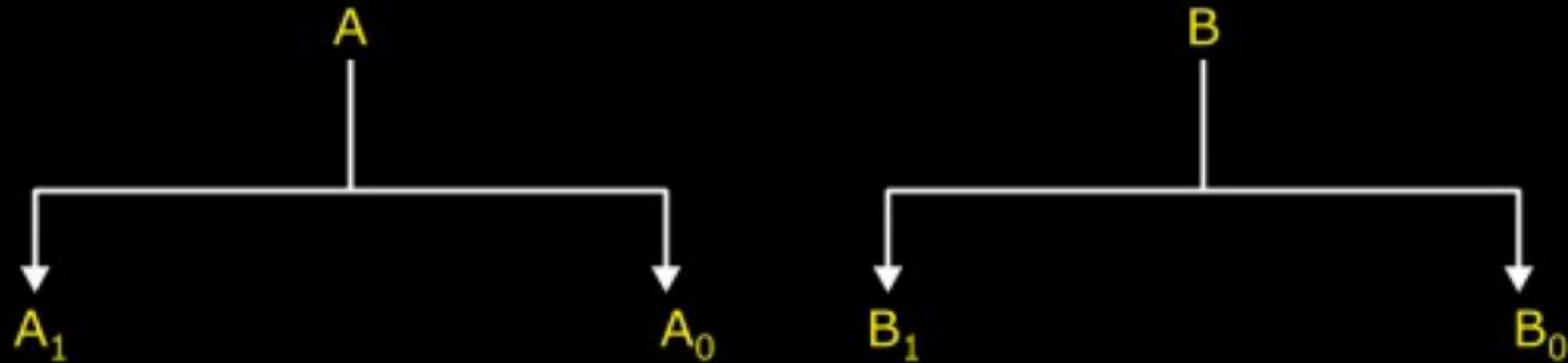SHORT TRICK TO USE SEMI MINIMIZED EXPRESSION



Thank you

GW
Soldiers!

