## CS & IT



## ENGINEERING



Combinational Circuit

Lecture No. 5



By- CHANDAN SIR



TOPICS TO BE COVERED

#### 01 DECODER

02 Question Practice


03 HA

04 FA

05 Discussion


#### 8×3 Encoder



 

74	16	15	I4	Ls	L	I,	L	2	3,	y.
				O						_
				0						
0	0	0	0	0	1	0	0	0	1	0
6	O	6	0	1	0	0	0	0	1	1
0	0	0	t	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	L	0	1
O	1	0	0	0	0	0	O	1		
1	0	0	O	0	O	0	0	1	1	1
 
$$3 = 14 + 15 + 16 + 17$$
 $3 = 14 + 15 + 16 + 17$ 
 $3 = 15 + 13 + 16 + 17$ 
 $3 = 17 + 13 + 15 + 17$ 
 $3 = 17 + 13 + 15 + 17$ 



### LSB Priority Encoder:

LSB.

7	MSB			LSB		
	$I_3$	$I_2$	11	Lo	71	30
	X	×	Χ	1	0	0
	X	X	1	0	0	1
	X	1	0	0	J	0
	1	400	0	0	1	J
					7	






Recoder: A circuit which is use to convert Binary into any other code are called Recoder


 
#### DECODER


- 2 × 4 Decoder
- 3 × 8 Decoder
- 4 × 16 Decoder





#### 2 × 4 DECODER

Step 1.

 

#### Step 2.


I <sub>1</sub>	I <sub>0</sub>	<b>Ý3</b>	y <sub>2</sub>	<b>y</b> <sub>1</sub>	y <sub>0</sub>
0	0	0	0	6	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Step 3.


$$\lambda_2 = I_1 I_2$$

Step 4. Minimization  $\frac{\partial_3}{\partial t} = \mathcal{I}_1 I_0$ 

Step 5. Hardware Implementation

 



 



#### 3 × 8 DECODER


Step 2.

I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	<b>y</b> <sub>7</sub>	<b>y</b> <sub>6</sub>	<b>y</b> <sub>5</sub>	<b>y</b> <sub>4</sub>	<b>y</b> <sub>3</sub>	<b>y</b> <sub>2</sub>	<b>y</b> <sub>1</sub>	<b>y</b> <sub>0</sub>
0	0	0	0	0	0	O	0	0	0	1
0	0	1	σ	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	7	0	0
0	1	1	0	0	0	0	1	0	O	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	O	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	6

#### 3 × 8 DECODER

Step 4. Minimization


Step 5. Hardware Implementation

 






 
#### DESIGN 3 × 8 DECODER BY USING 2 × 4 DECODER



 



 




$$\frac{69}{8+1=9} + \frac{8}{8}$$

$$8+1=9$$

$$6 \times 64$$
Decoder


 
#### DESIGN 3 × 8 DECODER BY USING 2 × 4 DECODER



#### Q.1



A logic circuit consist of two  $2 \times 4$  decoders as shown in the figure.

The output of decoder are as follow:

$$D0 = 1$$
 when  $A0 = 0$ ,  $A1 = 0$ 


$$D1 = 1$$
 when  $A0 = 1$ ,  $A1 = 0$ 

$$D2 = 1$$
 when  $A0 = 0$ ,  $A1 = 1$ 

$$D3 = 1$$
 when  $A0 = 1$ ,  $A1 = 1$ 

The value of f(x, y, z) is

		A, Ao	03	Ds .	ם ט	0
A	0	00	0	0	0	1
		0	0	0	1	0
B	Z	10	0	1	0	0
	Z	-1 1	1	0	O	0

 



 
#### Q.2




The Boolean expression f(a, b, c) in its canonical form for the decoder circuit shown below is

- A Π M(4, 6)
- B  $\Sigma$  m(0, 1, 2, 3, 5, 7)
- Sm(4, 6) /
- **D** Π M(0, 1, 2, 3, 5)





 



$$f = \overline{c} \in \mathbb{E}m(3,4,6,7)$$

$$f = \overline{c} \left[ \overline{A},8c + AB\overline{c} + AB\overline{c} + AB\overline{c} + AB\overline{c} + AB\overline{c} \right]$$

$$f = AB\overline{c} + AB\overline{c}$$


$$\sqrt{f} = \overline{c} \in \mathbb{E}m(9,6)$$

$$\sqrt{f} = \mathbb{E}m(9,6)$$





# Besign Binary to Decimal Decoder?

 



#### HALF ADDER

Two bit adder are known as half adder.



#### HALF ADDER

#### Step 1.





#### HALF ADDER

Step 2. Truth table.

A	В	Sum	Carry
0	0	0	0
0	1	L	0
1	0	1	0
1	1	0	1



#### HALF ADDER

Step 3.

$$sum = \overline{AB} + A\overline{B} = A \oplus B$$


$$carry = AB$$


Step 4. Minimization



#### HALF ADDER


#### Step 5.

 

 




#### By NAND GATE

 




#### By NAND GATE

 


By NOR GLATE



 




 




### HALF ADDER BY Using 2X4 Decoder ->

 

## Pw

#### **FULL ADDER**

Three bit adder are known as full adder

 

$$\begin{array}{c|c}
0 & 0 & 1 \\
+0 & +1 & +1 \\
\hline
0 & 0 & 1
\end{array}$$
Corry
Corry
Corry

when majority of

the inputs are

#### **FULL ADDER**

Step 2.

	A	В	С	Sum	Carry
0	0	0	0	0	0
J->	0	0	1	1	0
2	0	1	0	1	0
<b>3</b> →	0	1	1	0	1
47	1	0	0	1	0
<b>5</b> →	1	0	1	0	1
6-7	1	1	0	0	1
7-	1	1	1	1	7

high.




#### FULL ADDER

Step 3. Sum 
$$(A, B, C) = \leq m(1, 2, 4, 7) = A \oplus B \oplus C = (A \oplus B) \oplus C$$

Step 4. Carry (A, B, C) = 
$$\sum m(3,5,6,7) = ABC + ABC +$$




$$=(A\oplus B)C+AB$$

 






 





#### **FULL ADDER**

 

AST (ADA):C = CAYMY



HALF






A full adder is implemented with two half adders and one OR gate. OR gate is used to derive the final carry function of full adder. In each half adder,  $T_{sum} = 25$  ns and  $T_{carry} = 20$  ns and  $T_{OR} = 25$  ns. The minimum time required to derive both the sum and carry function of a full adder after applying the inputs is \_\_\_\_ ns





A logic function 'f' is implemented by the circuit shown in the figure below. The circuit consists of one 2×4 decoder, two 2×1 multiplexers and a two input or gate connected in cascade. Then the function f is equal to.

 - $A \oplus B$
- $B \rightarrow A \oplus B \oplus C$
- C B ⊙ C
- **D** A ⊙ B








What is the Boolean expression for the output f of the combinational logic circuit of NOR gates given below?

 - $\overline{Q+R}$
- $\overline{P+Q}$
- $\overline{C}$   $\overline{P+R}$
- $\overline{P+Q+R}$










The combinational circuit given below implements which of the following

 - A NOR gate
- B XOR gate
- C NAND gate
- None of these








The combinational logic circuit shown in the given figure has an output Q which is

 - A ABC
- B A + B + C
- $A \oplus B \oplus C$
- D A.B + C





# Thank you



