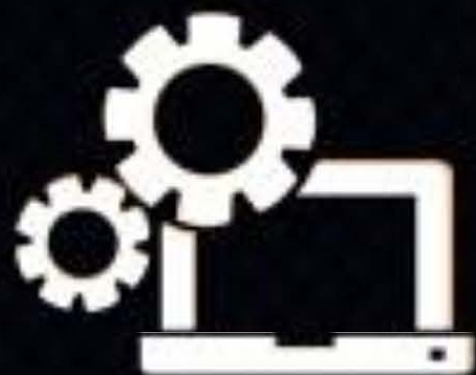


CS & IT ENGINEERING

Subject- Digital LOGIC
Chapter- LOGIC GATE



Lecture No. 3



By- CHANDAN SIR



01 AND, OR GATE

02 NAND GATE

03 NOR GATE


04 Discussion

**Minimum no. of NAND
NOR GATE**


NAND/NOR

→ universal Logic

✓ X-OR GATE

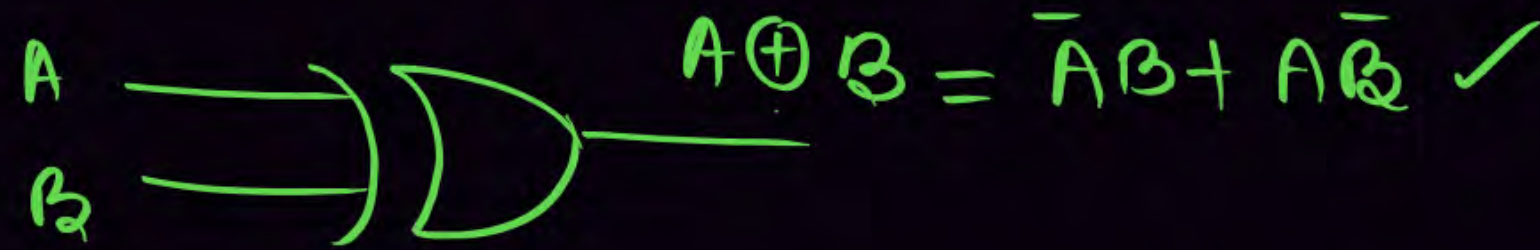

✓ X-NOR GATE

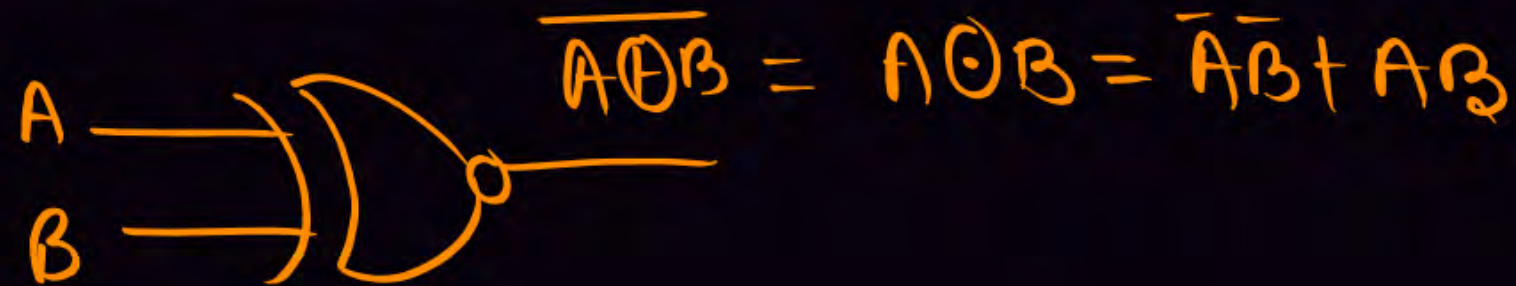

NOT GATE.



$$f = \frac{1}{2N \times \tau_{pd}}$$

AND




OR



NAND



NOR

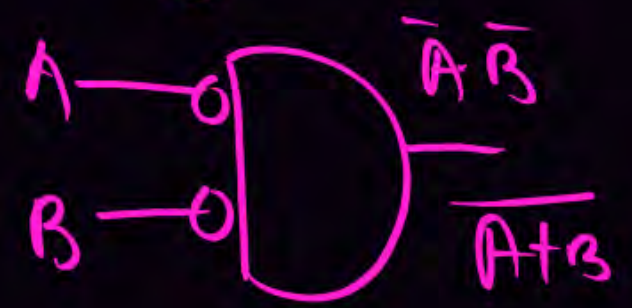

TTL

floating terminal = 1

ECL

floating terminal = 0

$$\overline{AB} = \bar{A} + \bar{B}$$

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

Distribution Theorem

$$A + B \cdot C = (A + B)(A + C)$$

$$A + B \cdot C \cdot D = (A + B)(A + C)(A + D)$$

Question \rightarrow

$$\begin{aligned} \textcircled{1} \quad A + \bar{A} \cdot \bar{B} &\Rightarrow (A + \bar{A})(A + \bar{B}) \\ &\Rightarrow 1 \cdot (A + \bar{B}) \\ &\Rightarrow A + \bar{B} \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad \bar{A} + A \cdot B &= (\bar{A} + A)(\bar{A} + B) = 1 \cdot (\bar{A} + B) \\ &= \bar{A} + B \end{aligned}$$

$$A + \bar{A} = 1$$

$$A \cdot \bar{A} = 0$$

$$A \cdot A = A$$


$$A + A = A$$

$$\bar{A} + 0 = \bar{A}$$

$$A + 0 = A$$

$$\begin{aligned} \overline{A} + AB &= (\overline{A} + A)(\overline{A} + B) \\ &= \overline{1}(\overline{A} + B) \Rightarrow \overline{A} + B \end{aligned}$$
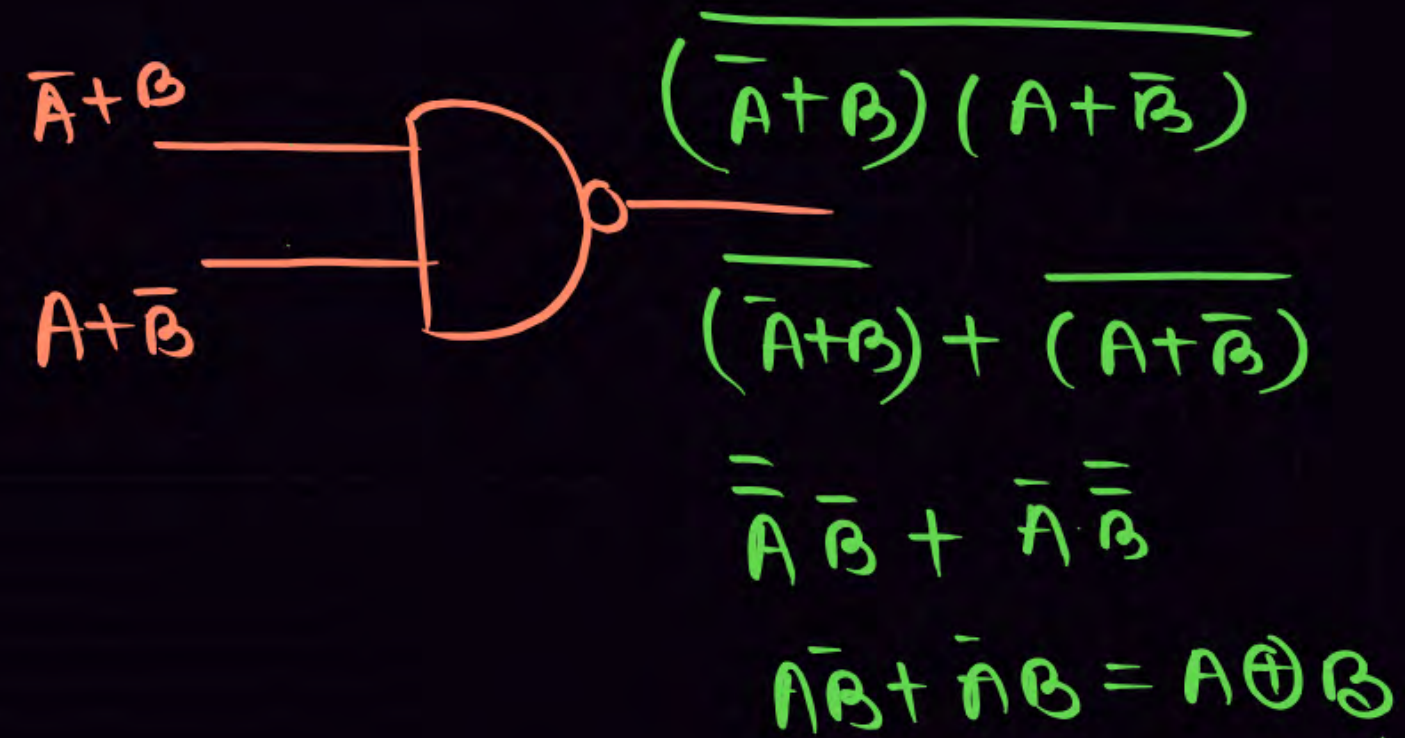
$$\begin{aligned} \overline{B} + AB &= (\overline{B} + A)(\overline{B} + B) \\ &= (A + \overline{B}) \cdot 1 \\ &= A + \overline{B} \end{aligned}$$




NAND AS A UNIVERSAL LOGIC :->


① NOT GATE :->




② AND GATE :->

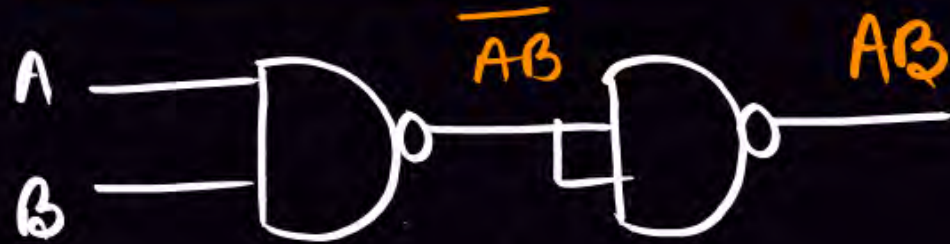


③ OR GATE :->

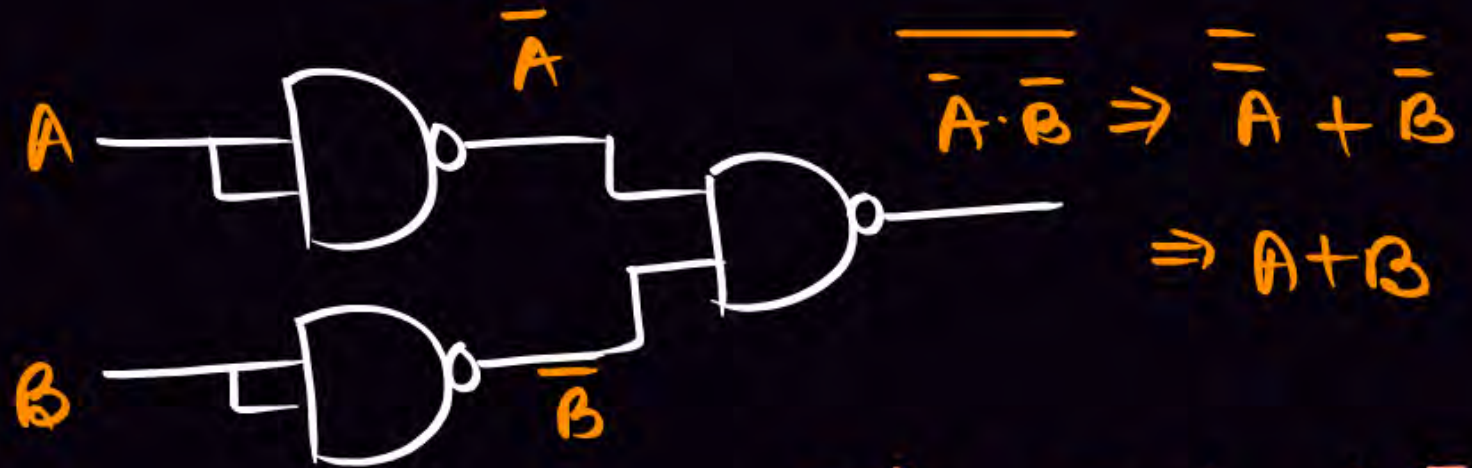


④ X-OR GATE :->

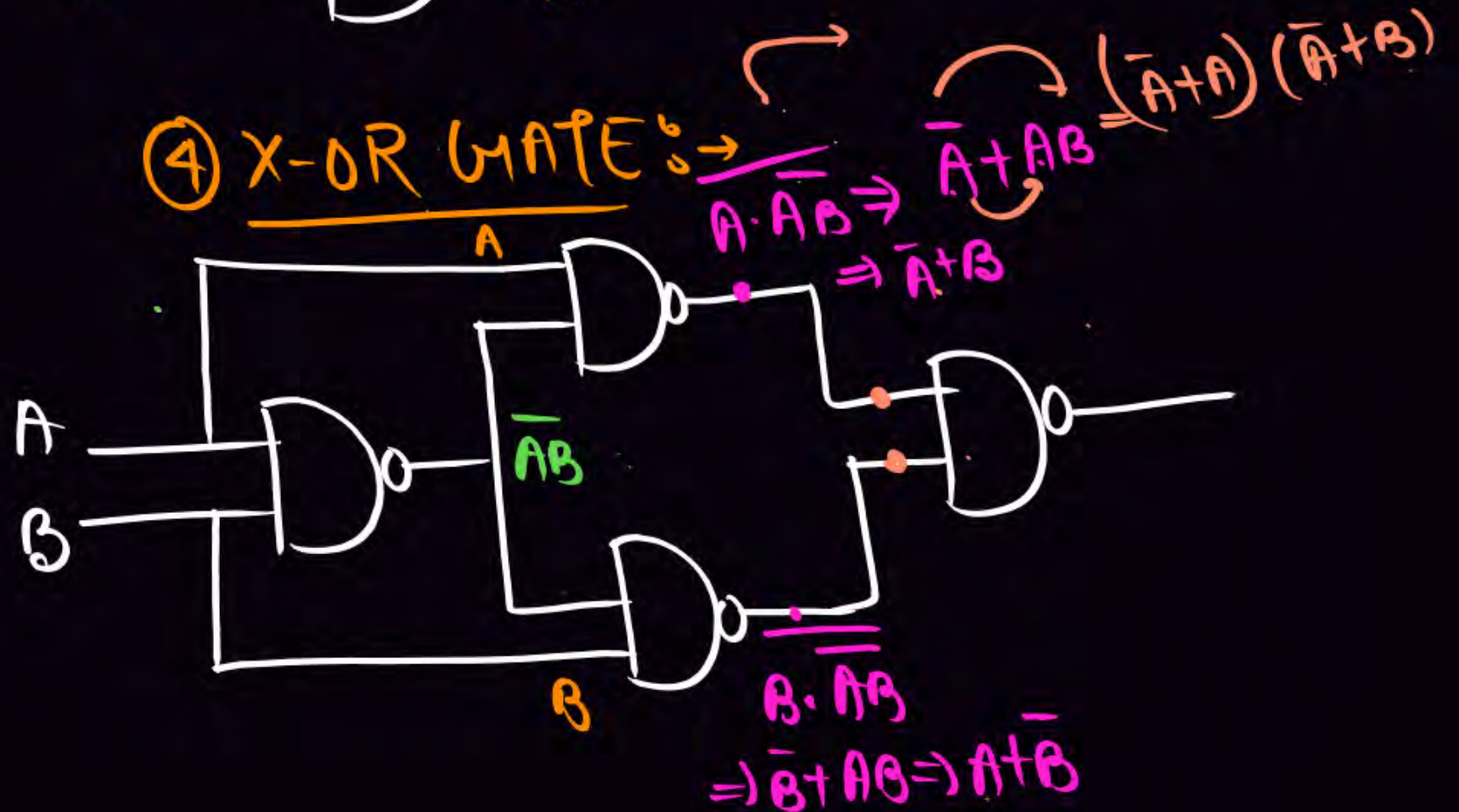

⑤ X-NOR GATE

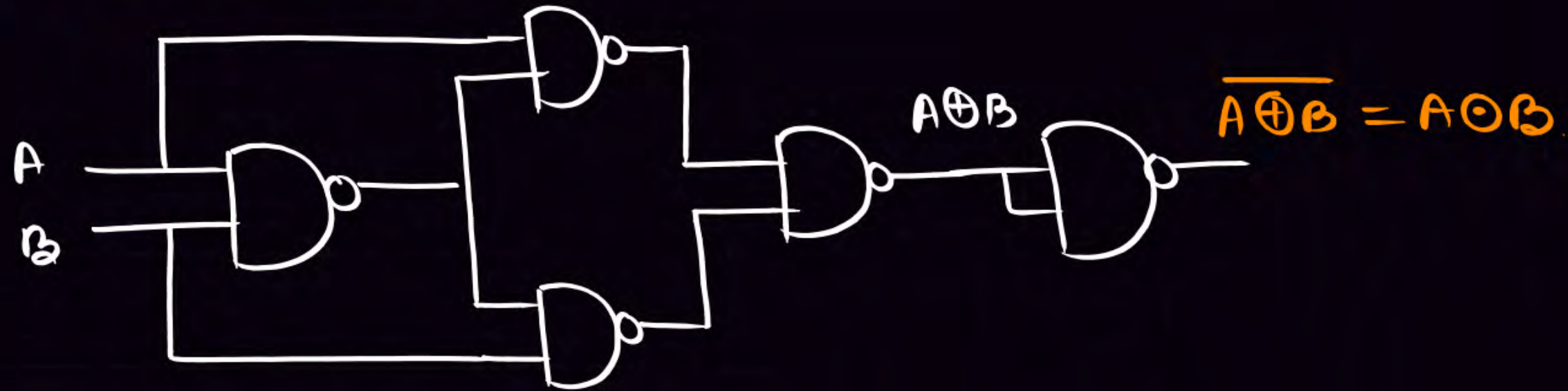

⑥ NOR GATE

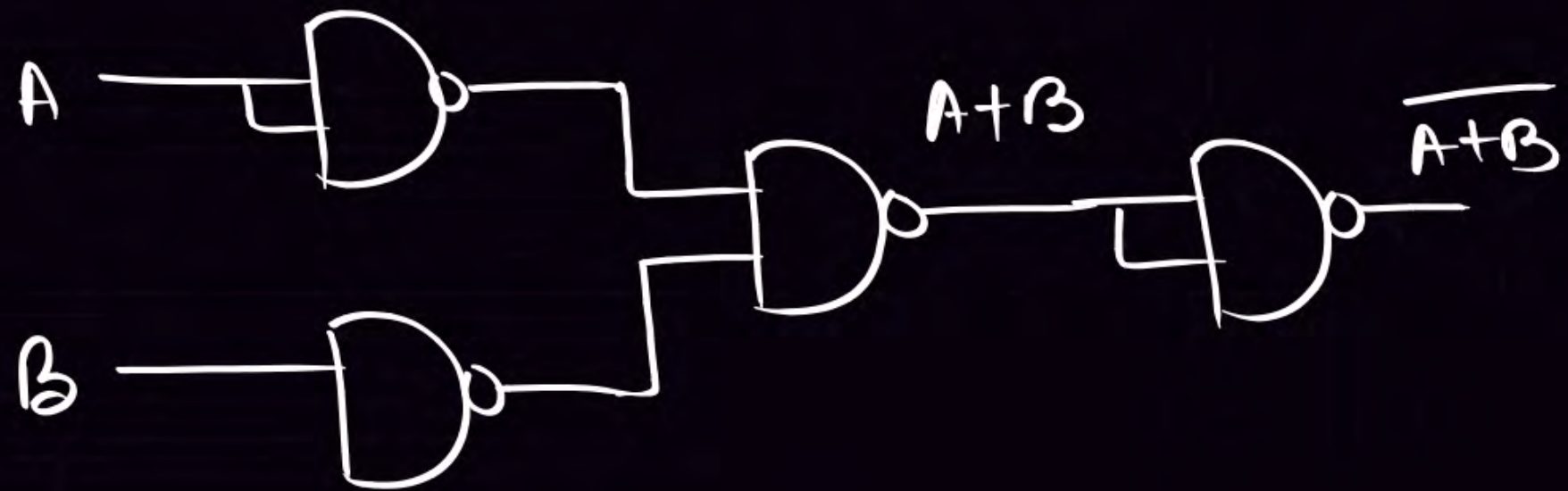



The table is decorated with red hearts and yellow stars. A heart with a star is at the top left. A row of five hearts is at the top. A circle of twelve stars is on the right. A heart is at the bottom right. A heart and a star are at the bottom left.

		NAND	NOR
★	NOT	1	1
★	AND	2	3
★	OR	3	2
★	X-OR	4	5
★	X-NOR	5	4
★	NAND	1	4
★	NOR	4	1

Q.1

MCQ



Which of the following option is called universal logic?

A NAND

B NOR

C Both A & B ★

D None

Q.2

MCQ



Which of the following option is called universal logic?

- ☒ A NAND
- ☐ B NOR
- ☐ C AND
- ☐ D OR

Q.3

MSQ ✓



Which of the following option(s) is/are called universal logic?





☒ A $(\overline{A+B}) \rightarrow \text{NOR}$


☒ B $(\overline{A \cdot B}) \rightarrow \text{NAND}$

☒ C $(A + \overline{B})$


☒ D $A \cdot \overline{B}$

$$A + \bar{B}$$

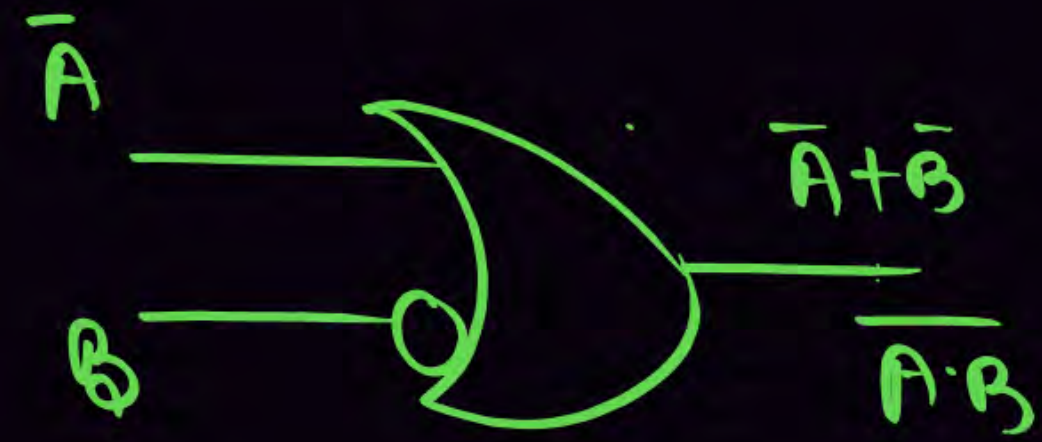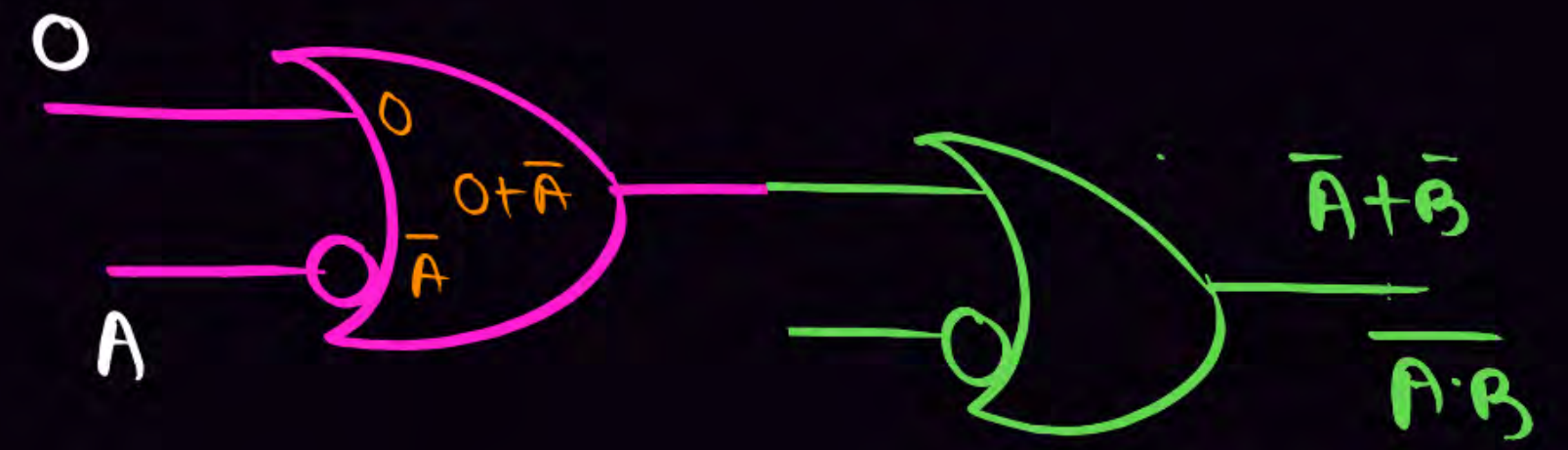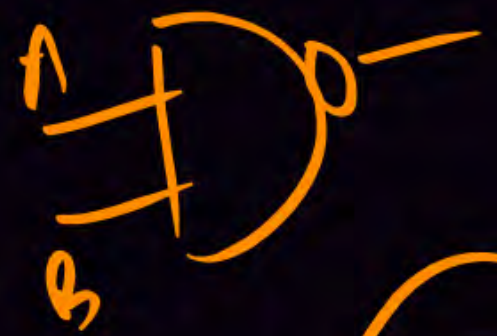
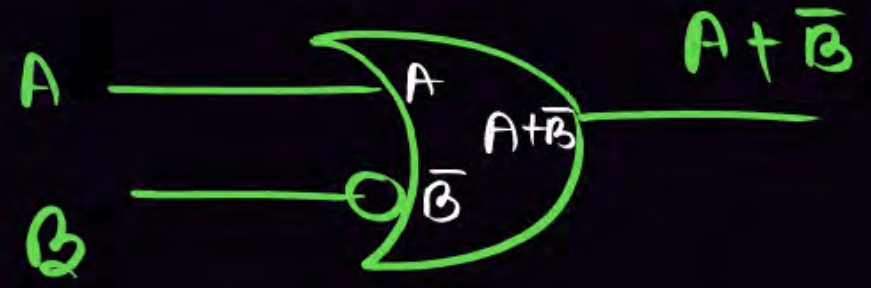


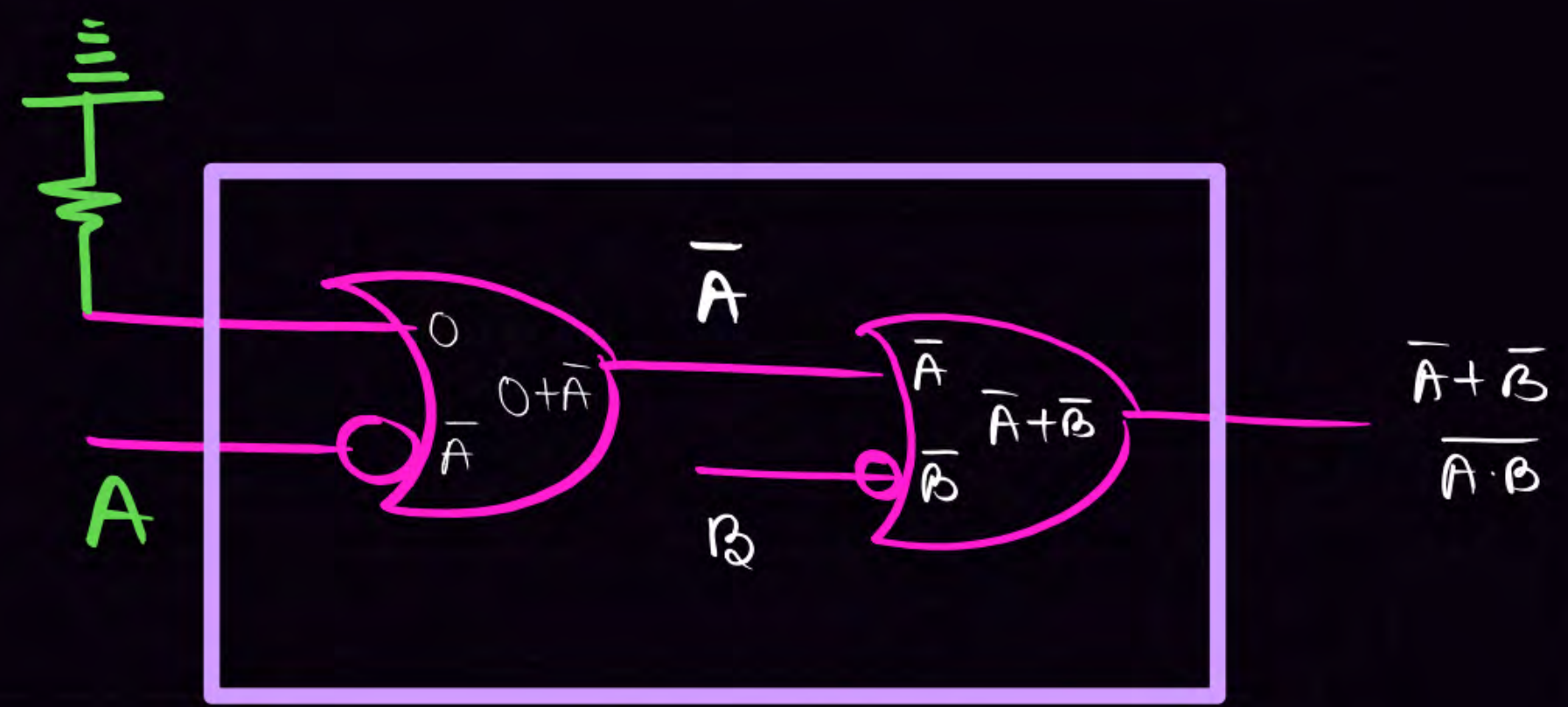


NAND

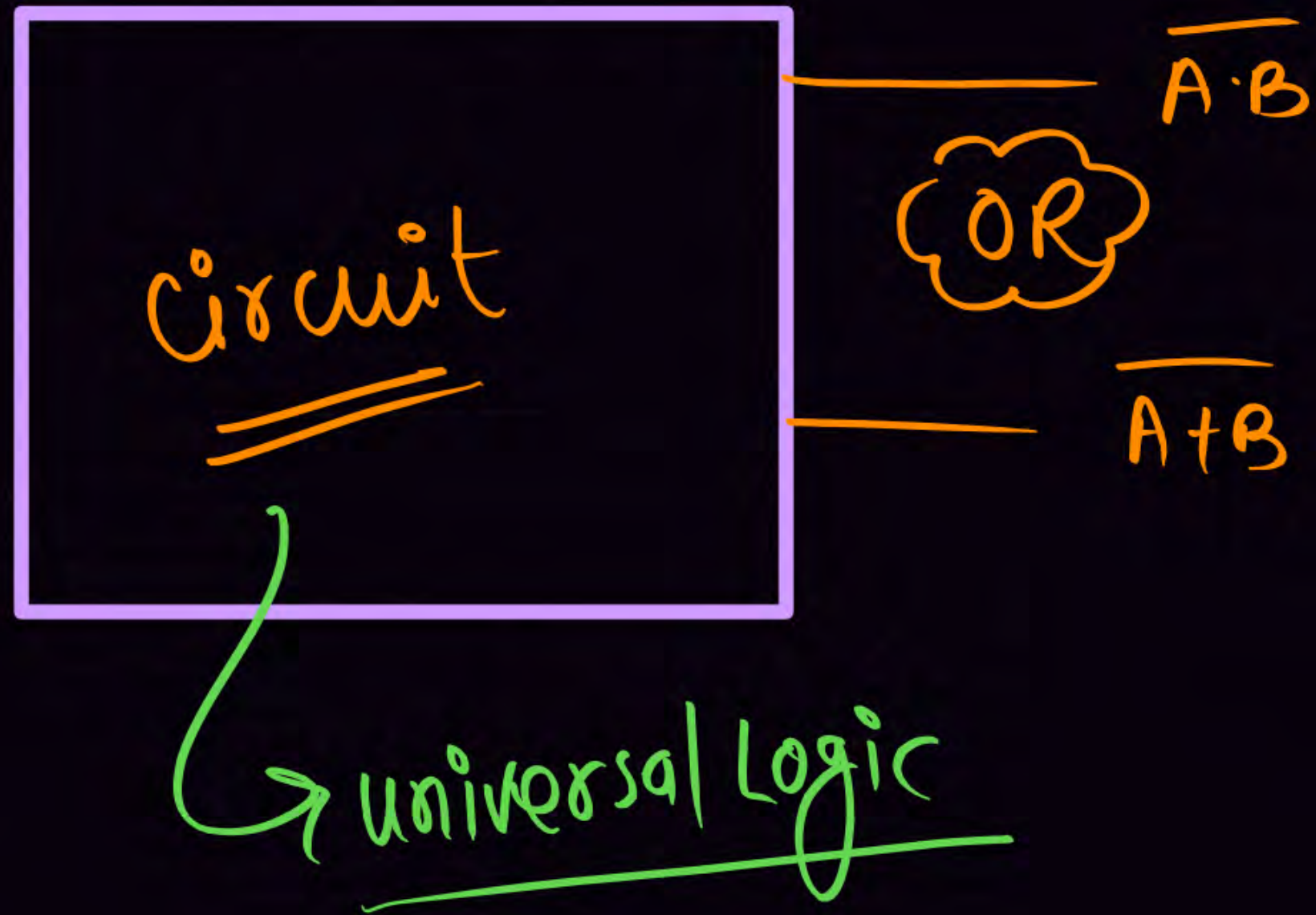


$$A \cdot \bar{B}$$

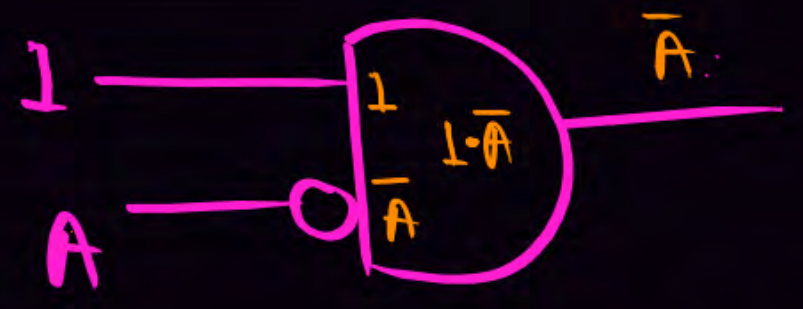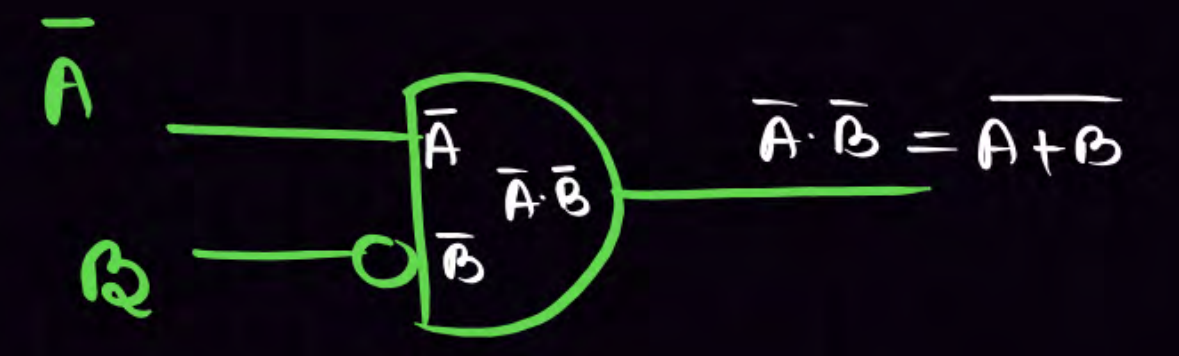

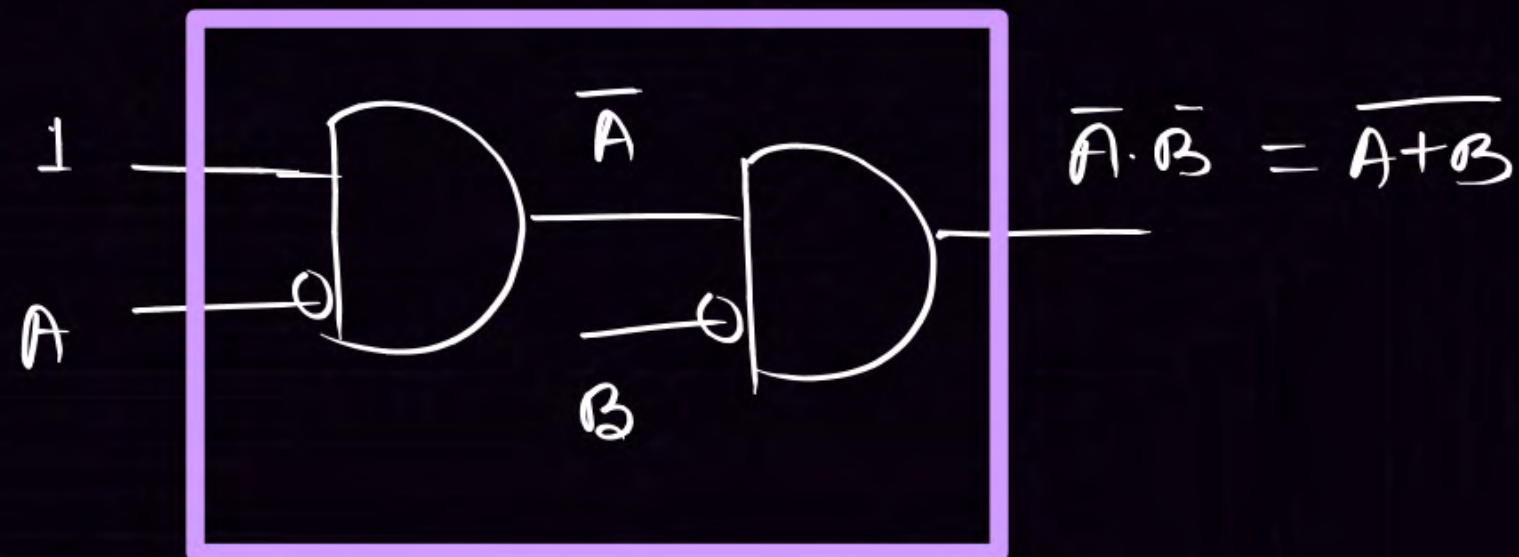

NOR
=

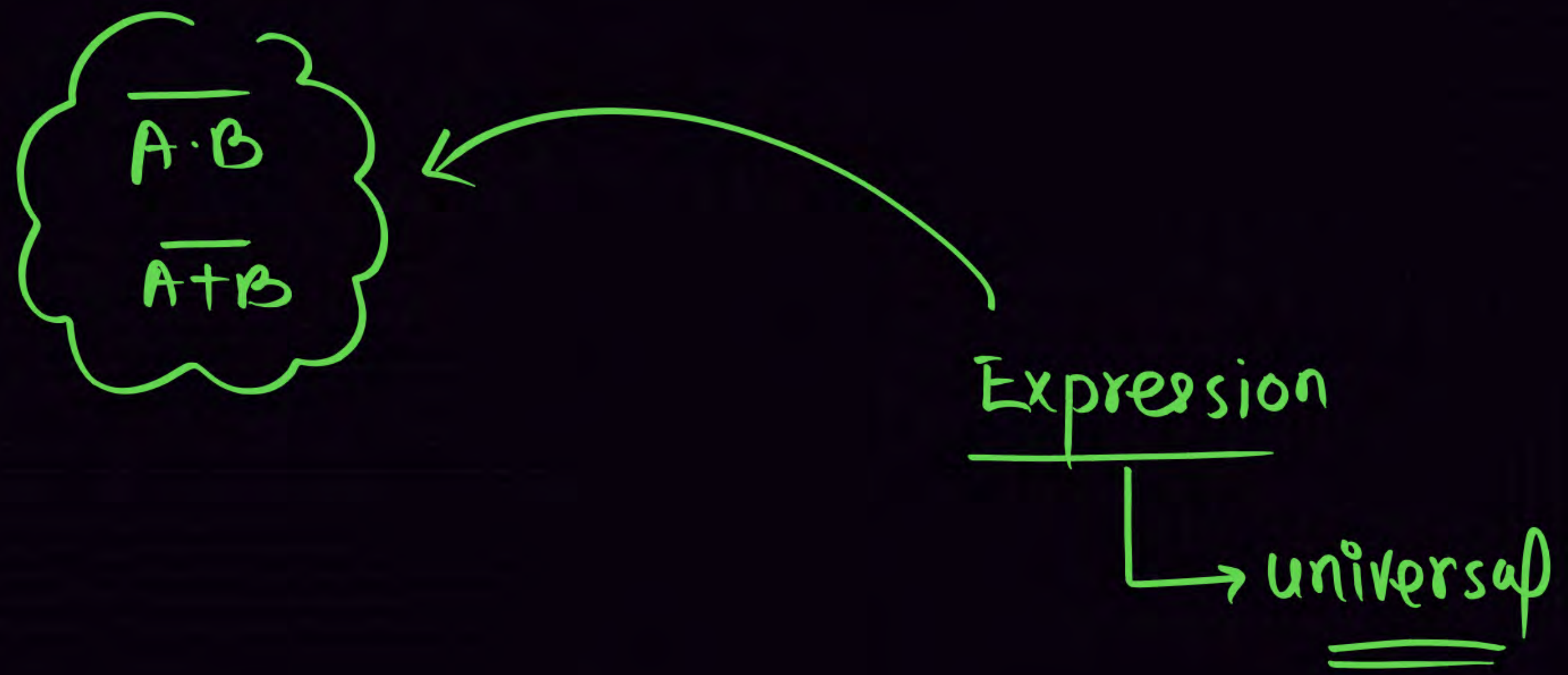

Universal Logic

$$\overline{A \cdot B}$$

$$\overline{A + B}$$

$$A \cdot \overline{B}$$

$$\overline{A} \cdot B$$

$$A + \overline{B}$$



$$\overline{A} + B$$

MUX

DECODER + OR


NAND, NOR GATE

▪ Alternate Symbol

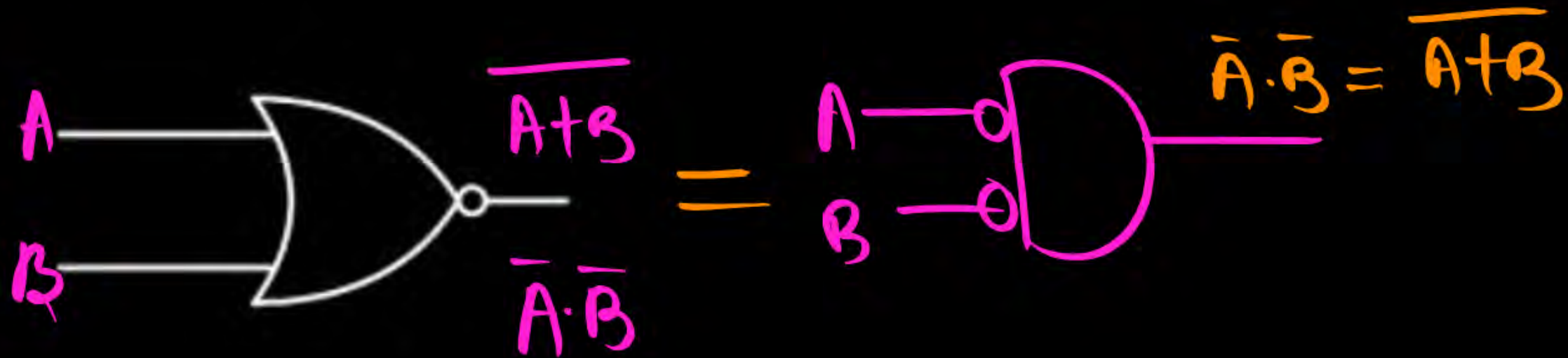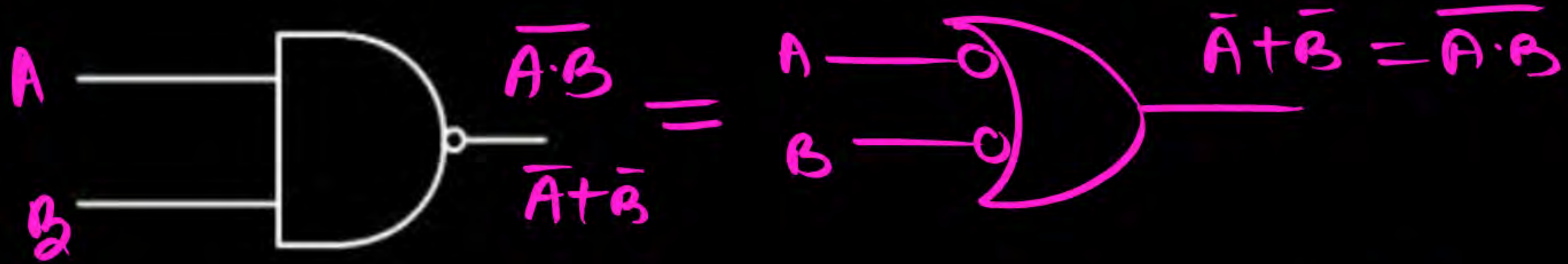


Q Find the minimum number of Two input NAND GATE required to Implement the function given below -

$$f(A, B, C) = \bar{A}BC$$

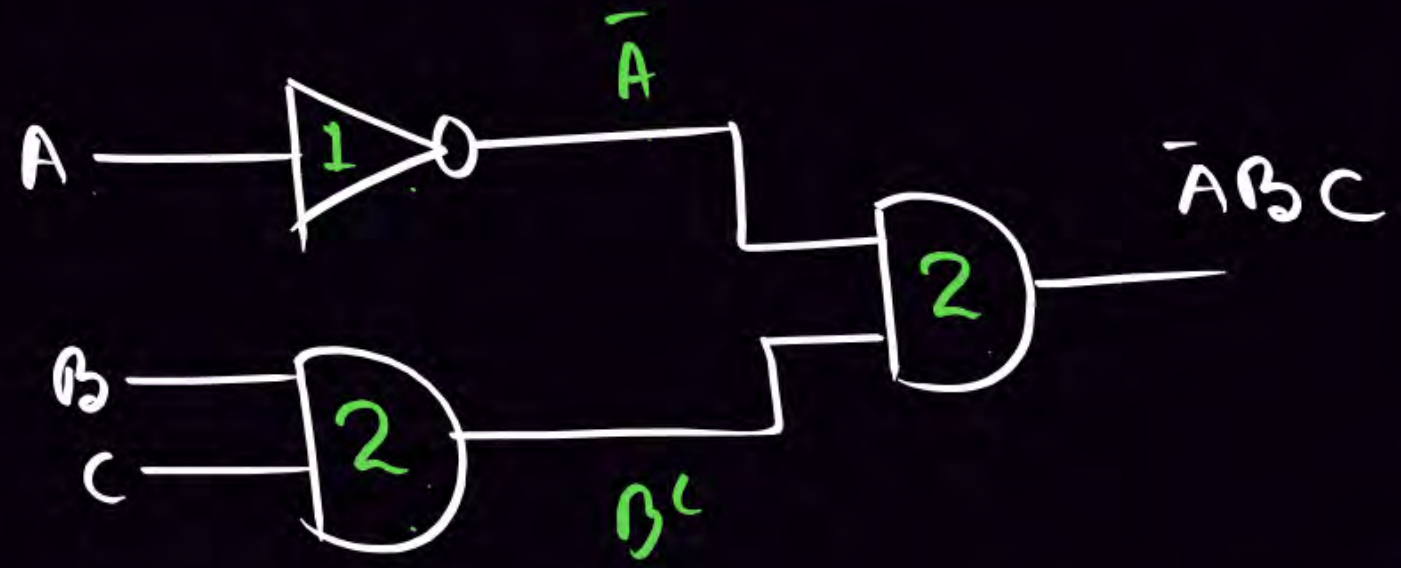

$$1 + 2 + 2 = \textcircled{5}$$

Ans

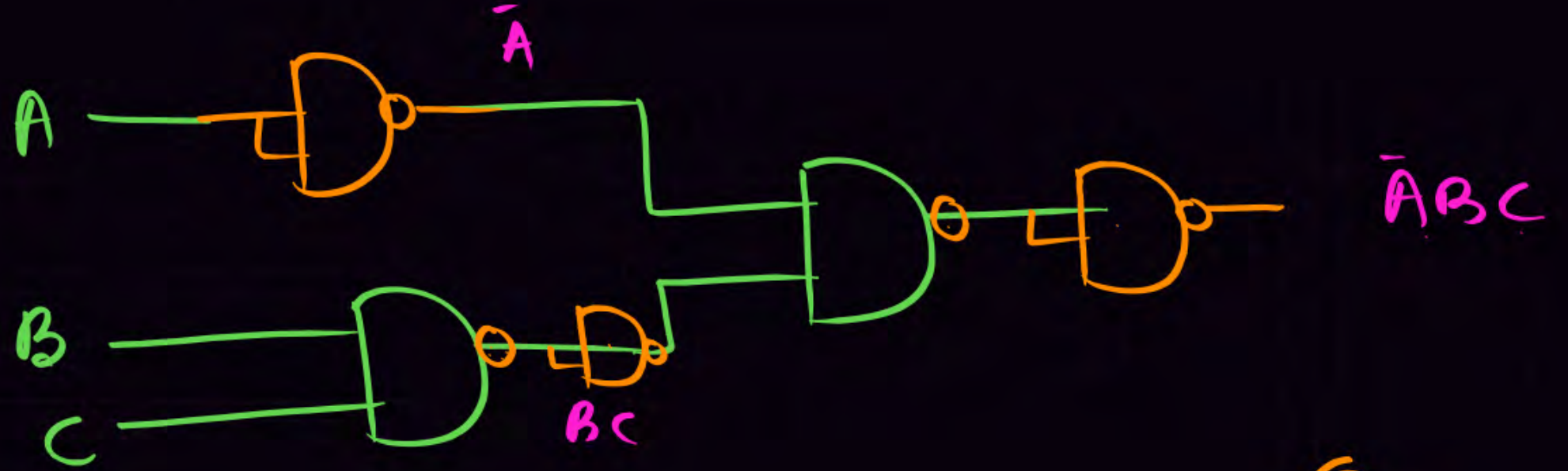

52

TYPE ①

$$f = \bar{A} \cdot B \cdot \bar{C} \cdot D \cdot E \cdot F \dots \dots \dots$$

Minimum no. of NAND = $(2n-2)+k$ Minimum no. of NOR = $(3n-3)-k$

$n \rightarrow$ Total no. of Variables

$k \rightarrow$ Total no. of complement Variables



Ex $f = \bar{A} B C$

NAND
$(2n-2)+k$
$n=3 \quad k=1$
$(2 \times 3 - 2) + 1$
<u>5</u>

NOR
$(3n-3)-k$
$n=3 \quad k=1$
$(3 \times 3 - 3) - 1$
<u>5</u>

$$f = \bar{A}BC$$

NOR = ?

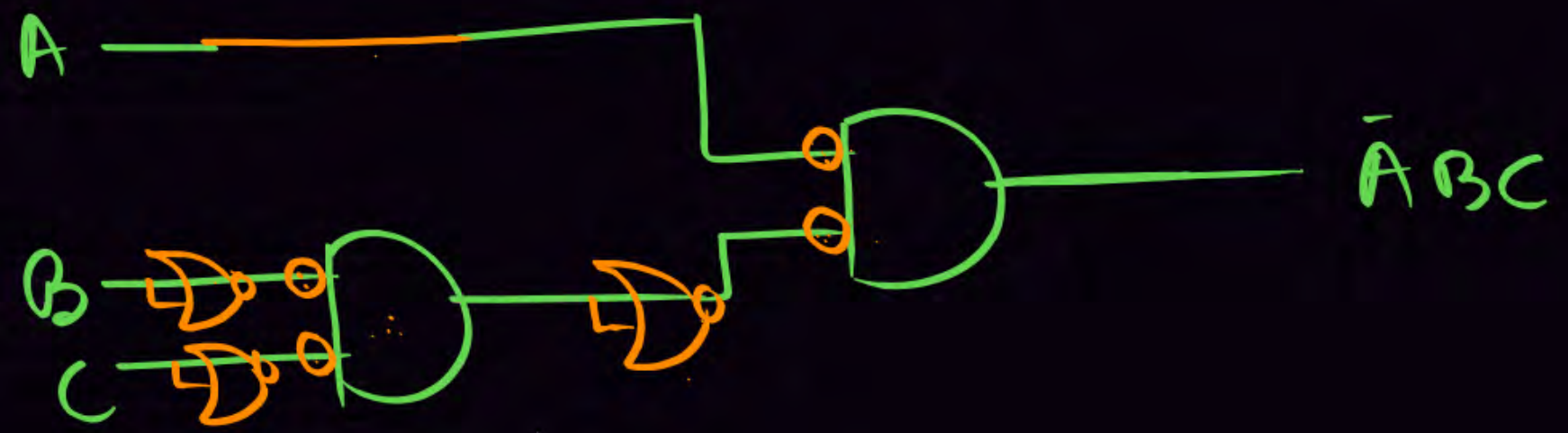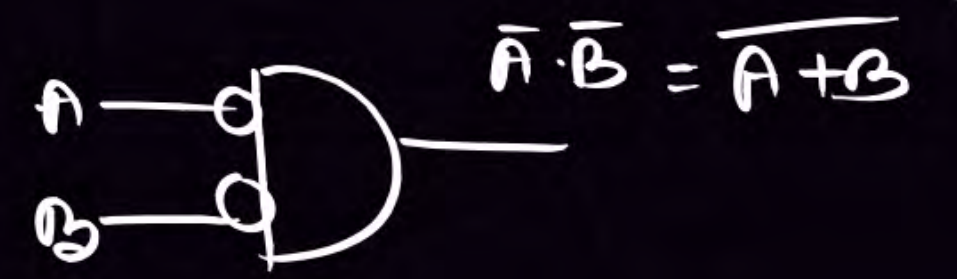

Ans = 5

$$f = \bar{A} \cdot B \cdot \bar{C} \cdot D$$

$$n=4 \quad k=2$$

$$NAND = (2n - 2) + k$$

$$(2 \times 4 - 2) + 2$$

$$\underline{\underline{8}} \text{ Ans}$$

$$NOR = (3n - 3) - k$$


$$= (3 \times 4 - 3) - 2$$

$$\Rightarrow 12 - 3 - 2$$

$$\Rightarrow \underline{\underline{7}} \text{ Ans}$$

$$f = \bar{A}B\bar{C}D$$


NAND

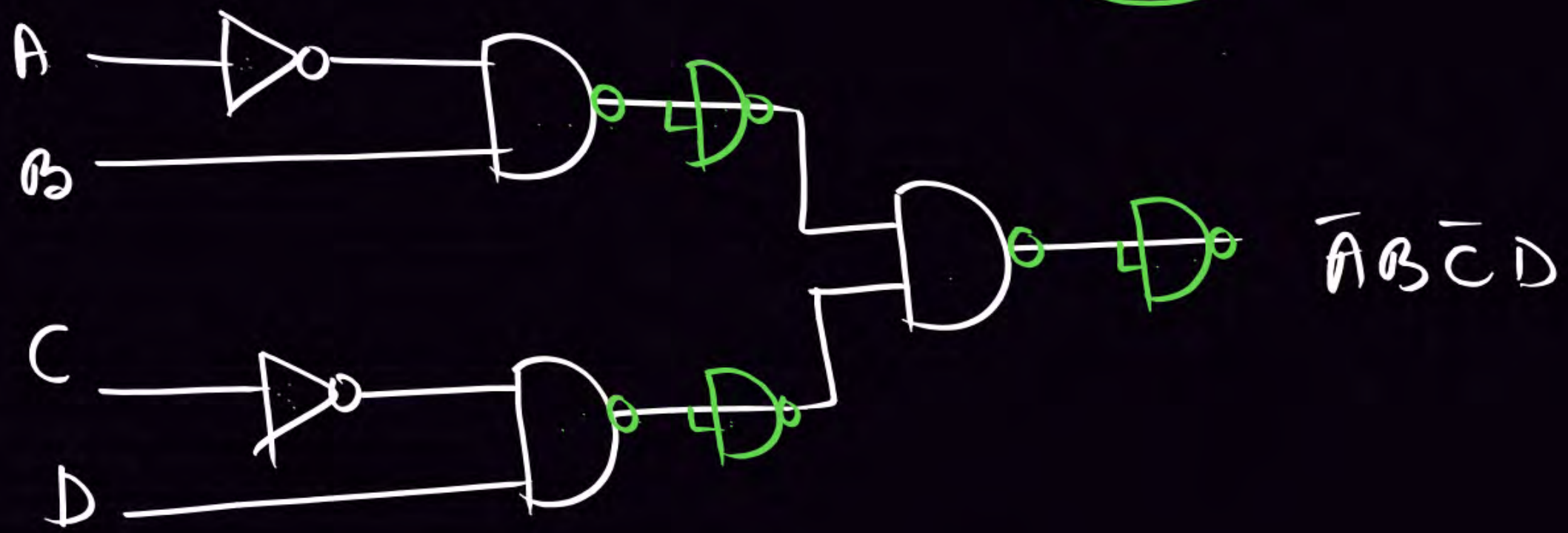

8
Ans

$$f = \bar{A}B\bar{C}D$$

(NOR)

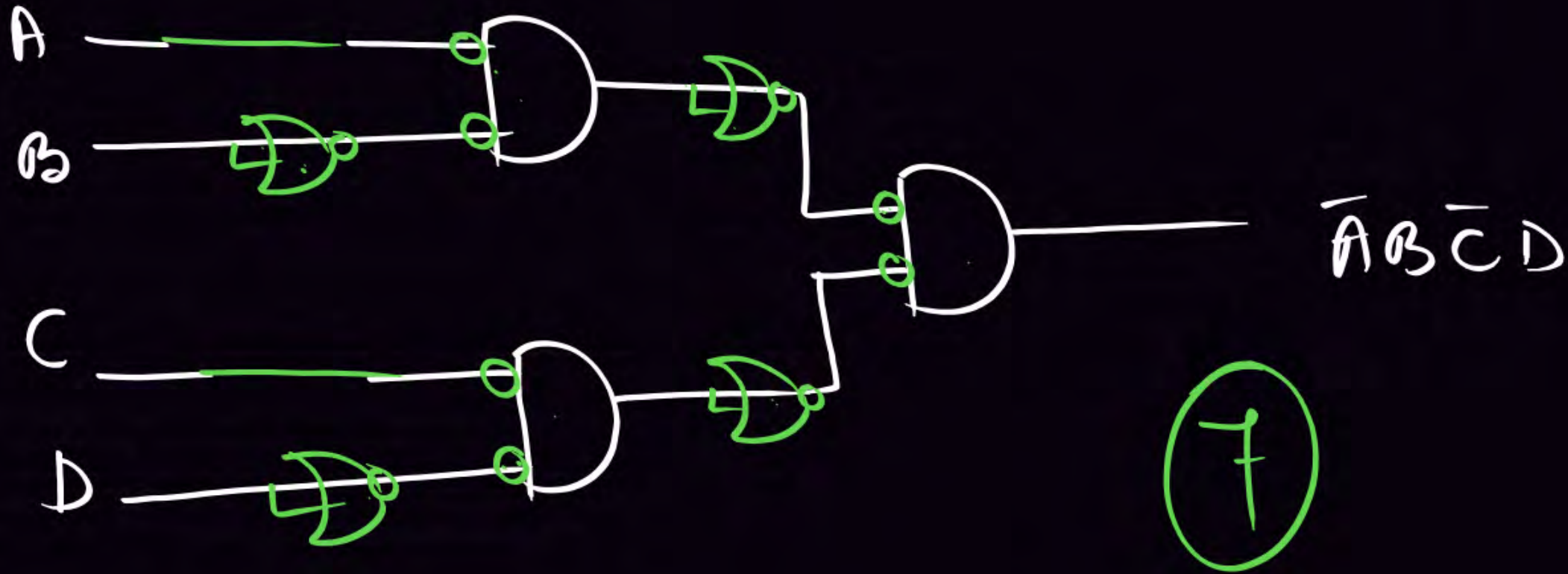

HW

$$f = \bar{A} \bar{B} \bar{C} D E$$

$$\text{NAND} = ?$$

$$\text{NOR} = ?$$

Thank you

GW
Soldiers !

