
CS & IT

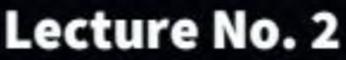





Digital Logic



Logic Gate



By- CHANDAN SIR



TOPICS TO
BE
COVERED


01 AND, OR GATE

02 NAND GATE

03 NOR GATE

04 Discussion

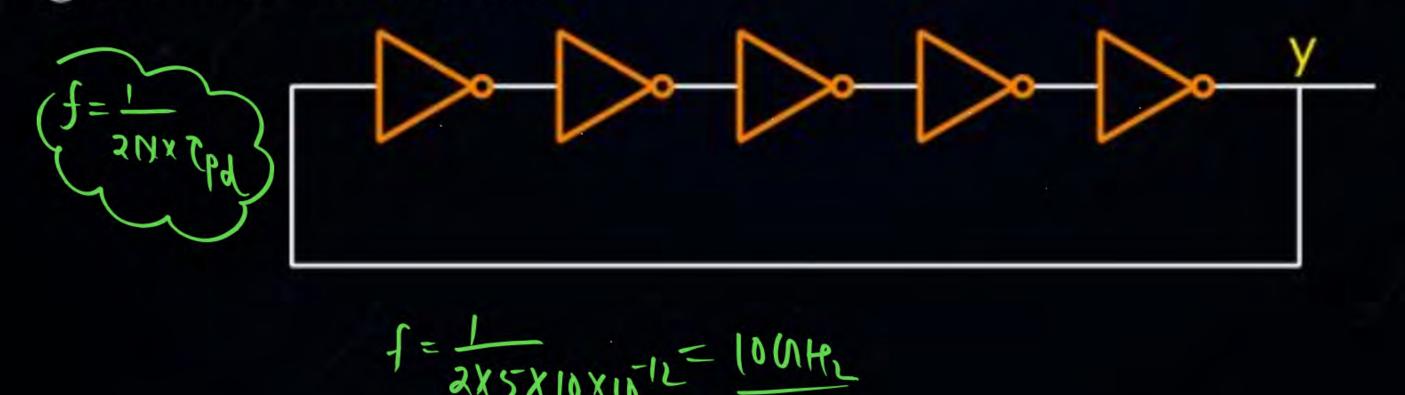For the circuit given below, all NOT Gates are identical to each other and having propagation delay 10 ps. Find the frequency of generated wave form?







Circuit given below are called.







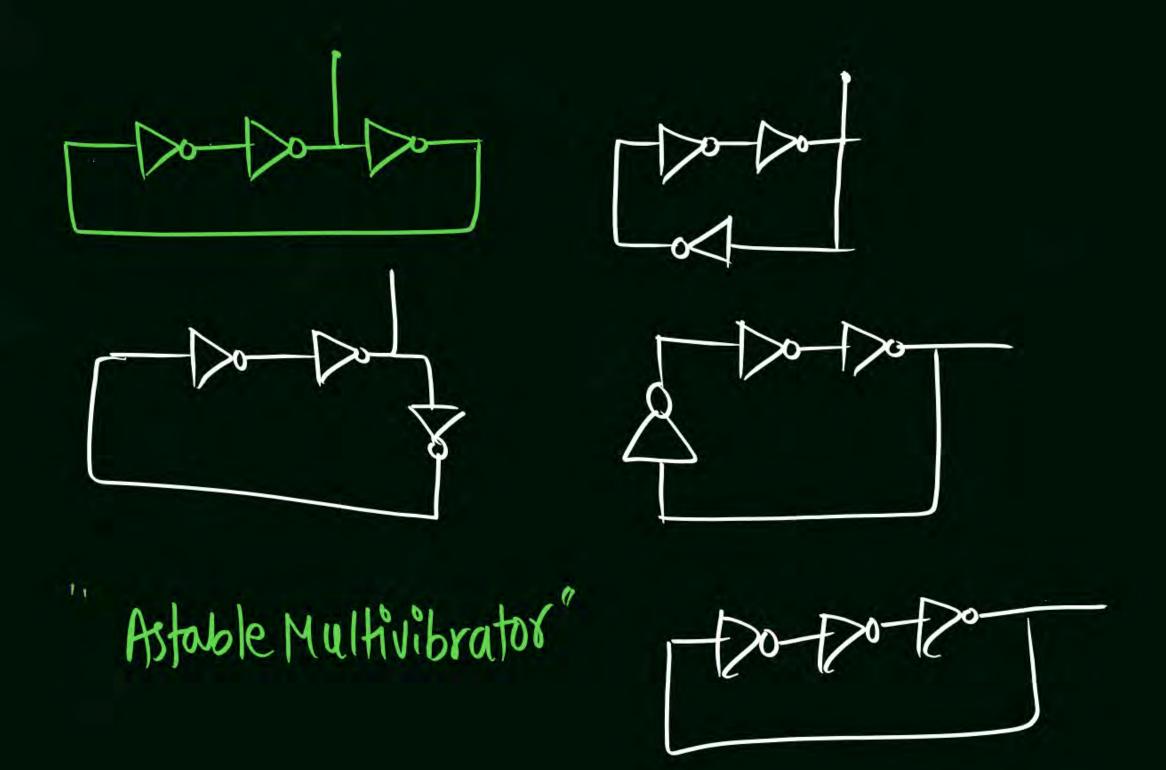



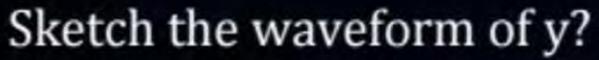

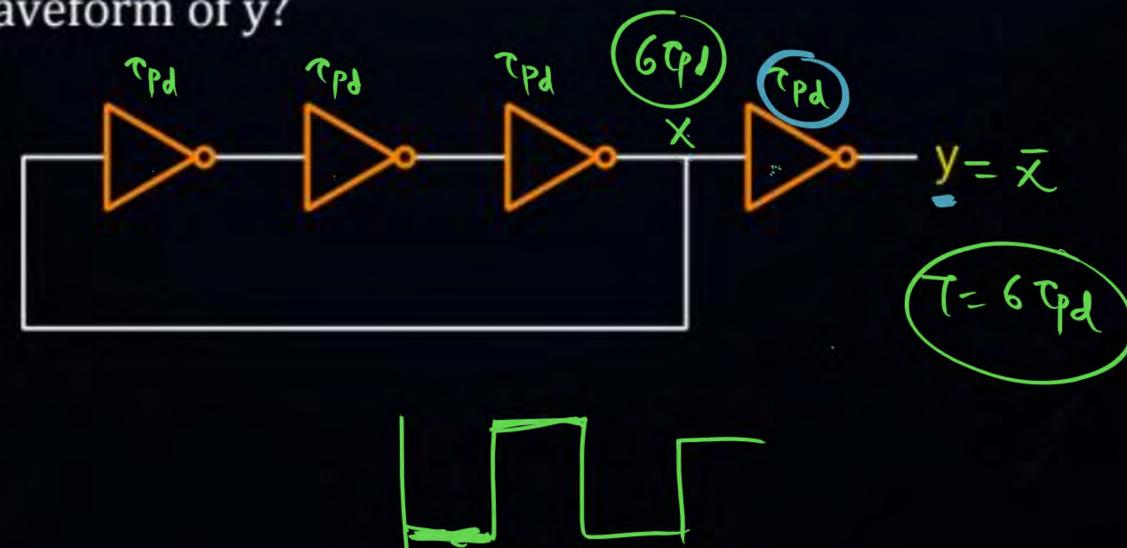

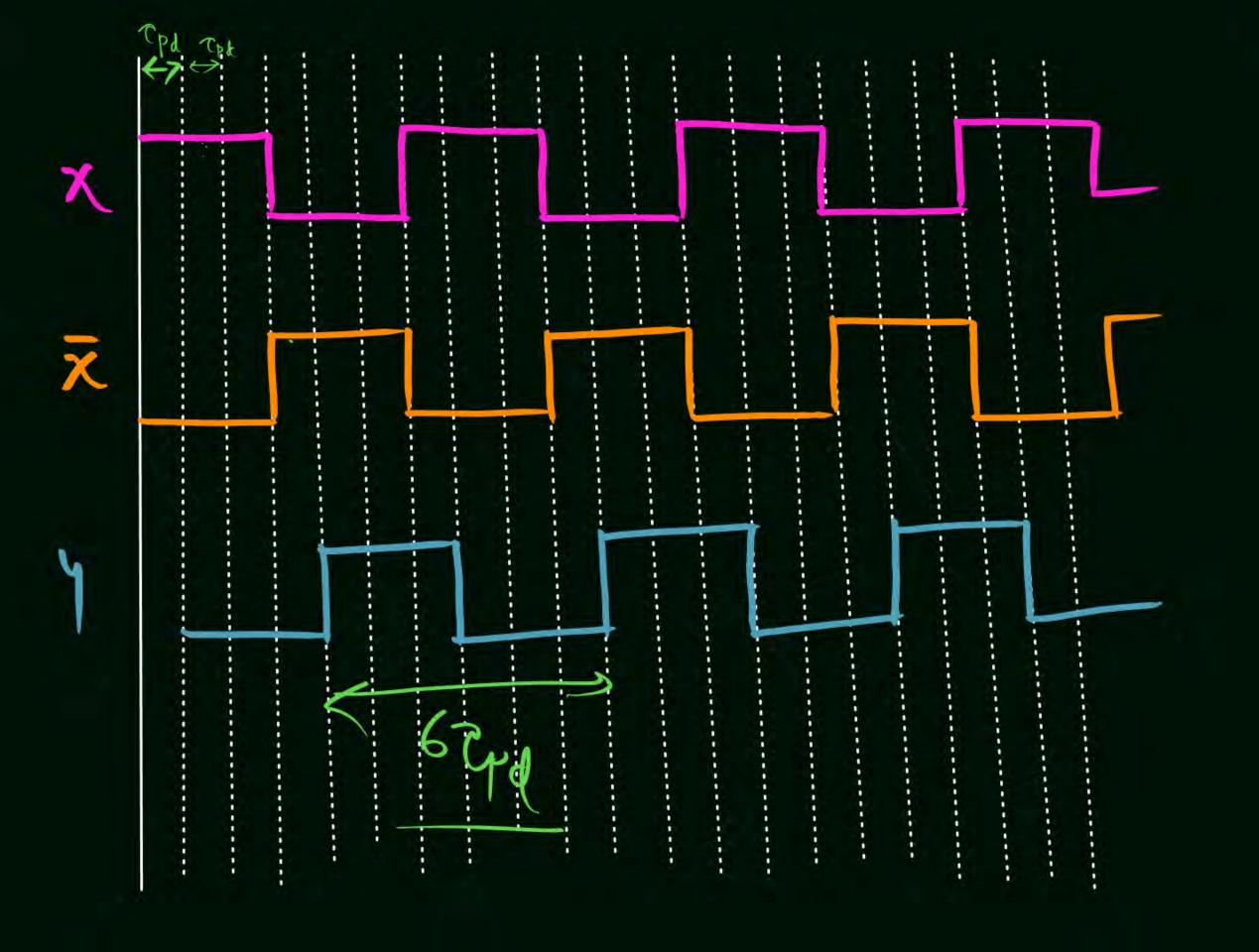






For the circuit given below x & y condition will be-

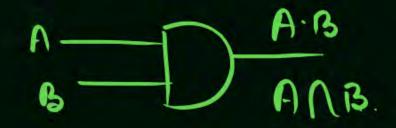- A x stable y toggle
- B x toggle y stable
- x & y both toggle
- x & y both stable









AND [N]

$$\dot{O} \cdot O = O$$

$$O \cdot \Gamma = O$$

$$1.0 = 0$$

$$1 \cdot 1 = 1$$

$$A = A \cdot 1$$

$$\bar{A} = \bar{A} \cdot 1$$

$$A.0 = 0$$

$$\bar{A} \cdot 0 = 0$$

$$A - A$$

$$0+7=1$$
$$0+0=0$$

$$1 = 0 + 1$$

[リ]

$$1 + A = 1$$

$$1+\overline{A}=1$$

$$A + \bar{A} = 1$$



1+ AB = 1

AND GATE

AND GATE

Symbol

$$A \longrightarrow y = A.B$$

Symbol



-> Relation b/w inpuls & outputs.

Truth Table				
A	В	Y		
0	7 0	0		
0 <	1	0		
1	>> 0	0		
1	1	1		



3 Enable/Bisable:

$$A = 0,1$$

$$y = 0,0$$

Control'o' Disable

- I floating terminal
 - Control input
 - Strobe.

$$A=0,1$$

$$Y=0,1$$

Control '1' Enabled

AND GATE



Enable/Disable




4. Commutative Law

$$A. B = B. A$$

Associative Law A. B. C = (A. B). C



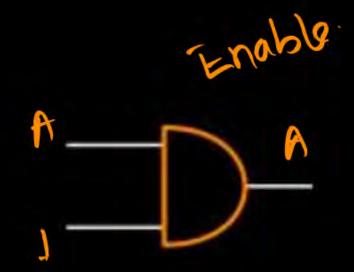



Associative Law

$$(A B) C = \Lambda(B C)$$



$$A \longrightarrow A \cdot L = A$$



when Legics are design by (TTY).

- (A) 1
- (B) O
- $(C)\overline{A}$

DA

(E) Sir, Mujhe nahi ata. Mai Tare jameen par hy.



(ECL) Emitter Coupled Logic

AND GATE



NOTE

- Whenever logic are designed by TTL (Transistor transistor logic) then floating terminal always works as a high.
- Whenever logic are designed by ECL (Emitter coupled logic) then floating terminal always works as a low.

OR GATE



$$E_{X}$$
. $\{1,2,3\}$

$$\begin{cases}
3,4,5
\end{cases}$$

$$\begin{cases}
43,4,5
\end{cases}$$



2- Truth table: >>

A	B	Y= F	+13
0	0	0	
0	1	1	
1	0	1	
1	1	1	

3 Enable/Bisable.

Control o Enable


Control : Aisabled.



commutative Law


$$(A+B)+C = A+(B+C)$$



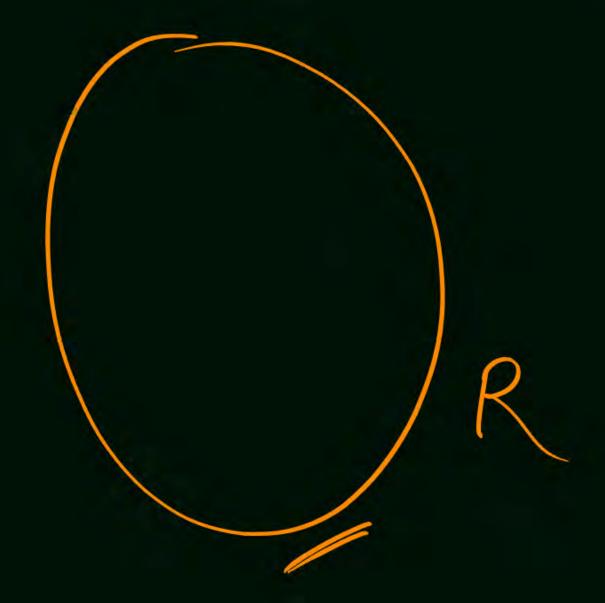



NAND GATE :->

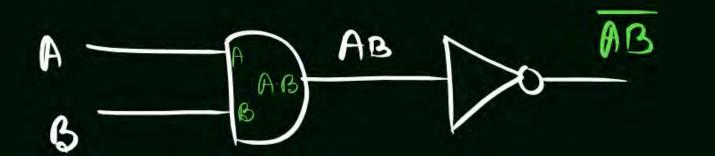

A:B = A+B Break the line, change the sign.

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$




$$\frac{A}{B} = \frac{A}{B} = \frac{A}{B} = \frac{A}{A+B} = \frac{A}{A+B}$$

NAND GATE



Symbol

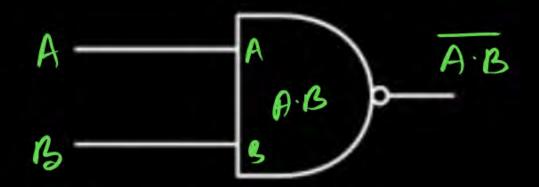


Truth Table

A	B	Y	A.B
0	70	1	
0	1	1	
1	0	J	
1	1	0	

NAND GATE




3. Enable/Disable

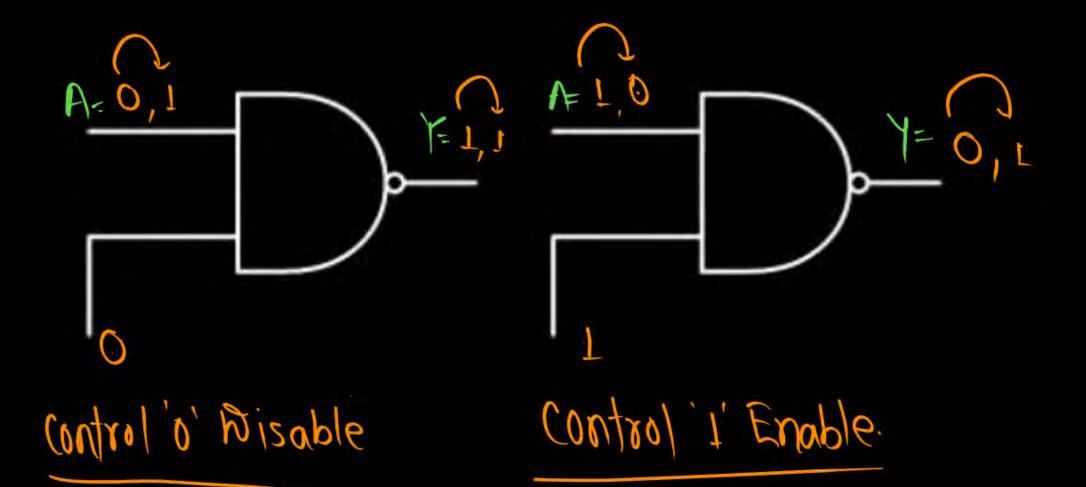

NAND GATE



4. Commutative Law

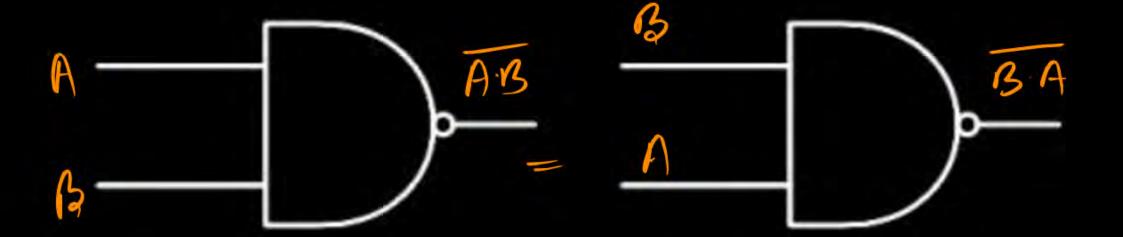




Associative Law

Hoes not follow associative Law

NOR GATE



Symbol

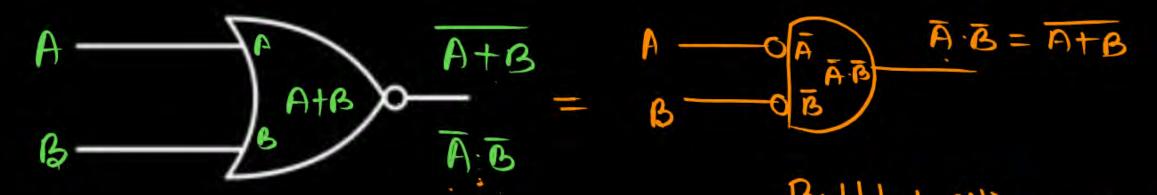

Bubbled AND = NOR


Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

NOR GATE

Pw

3. Enable/Disable

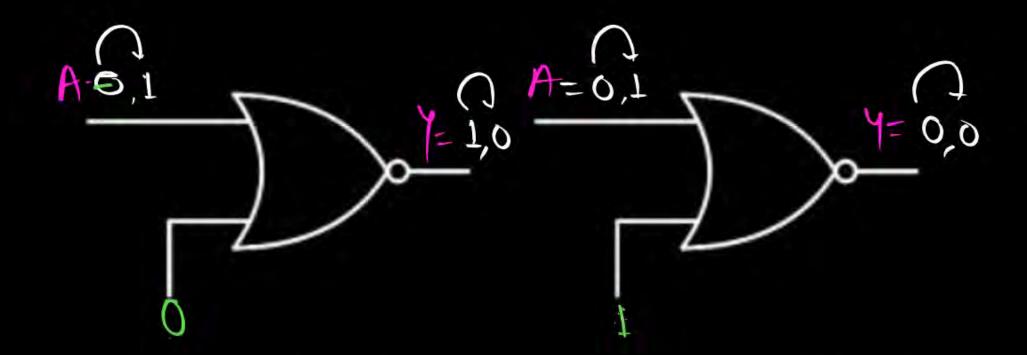

Control O'Enable

Control '1' Disabled.

NOR GATE



4. Commutative Law





Associative Law :- 7

$$A+B+C$$
 $A+B+C$
 $A+B+C$
 $A+B+C$
 $A+B+C$
 $A+B+C$
 $A+B+C$


Moes not follow associative Law



A HAND)
NOR

Universal Logic

CAIR 23)

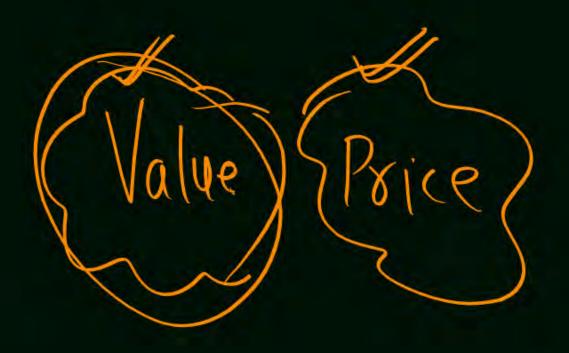



NOT AND A'B

 $f = \frac{1}{2NVT}$



Thank you

Seldiers!

