# CS & IT



# ENGINEERING



Sequential Circuit

Lecture No. 4



By- CHANDAN SIR



TOPICS TO BE COVERED 01 JK Flip Flop


**02** PRACTICE

**03** DISCUSSION

#### T-FF (Toggle FF)



#### 1) Symbol:-

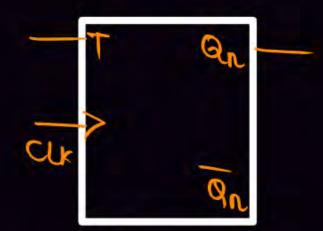

@ Truth table

| 7 | 9 <sub>nt1</sub> |
|---|------------------|
| 0 | Qn               |
| l | -Qn              |


3 char. Table

| + | Qn | Q <sub>n+1</sub> |
|---|----|------------------|
| 0 | 0  | 0                |
| 0 | 1  | 1                |
| 1 | 0  | 1                |
| L | 1  | 0                |

5 Excitation lable

| Qn | Qn+1 | + |
|----|------|---|
| 0  | 0    | 0 |
| 0  | 1    | 1 |
| L  | 0    | 1 |
| L  | 1    | O |

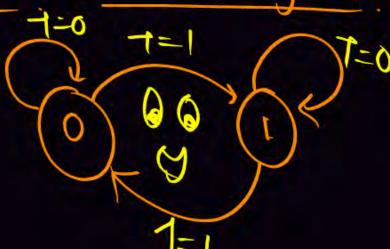1 Characteristic Equation 6 state Diagram








### Excitation Table

| Qn | 1410 | S | R | J | K | R | + |
|----|------|---|---|---|---|---|---|
| 0  | 0    | 0 | X | 0 | X | 0 | 0 |
| Ó  | 1    | 1 | 0 | J | × | 1 | J |
| Ŀ  | 0    | 0 | 1 | × | J | 0 | 1 |
| L  | 1    | X | 0 | × | 0 | 1 | 0 |



#### JK FF is also called universal FF.

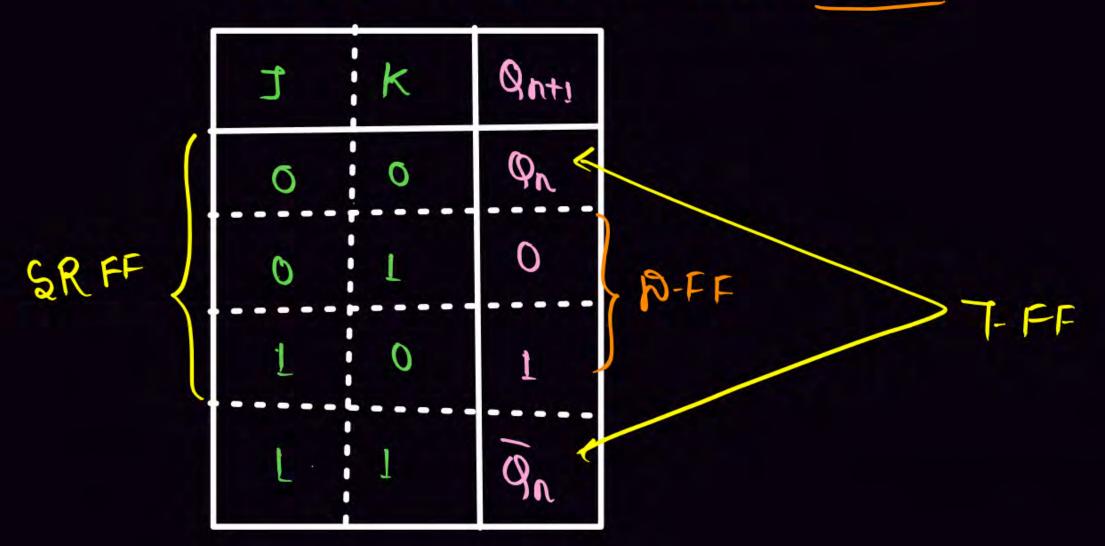

## pesigning of Flip-Flop:





Step 1: - Write the characteristic table of desired FF.

Step-2:- write the excitation table of avaliable FF

Step 3.: > Write the Logical Expression.

Step4:> Minimization

Step5:> Hardware Implementation.

#### Resired avaliable Aesign a JK FF by using SR FF.


Step1:>

| <b>フ</b> | K | Qn | Ou+1 | S  | R   | 5/ep3: → \$ (J,k,Qn) = Zm(4,6)+Zd(1,5)   |
|----------|---|----|------|----|-----|--|
| 0        | 0 | 0  | 0    | 0  | ×   | $R(J_1K_1Q_0)=Zm(3_17)+Td(0_12)$   |
| 0        | 0 | 1  | 1    | X  | 0   | Step 4 Minimization  |
| 0        | 1 | 0  | 0    | 0  | X   | S-TO IKON  |
| 0        | 1 | 1  | 0    | 0  | 1   | S⇒ 0 01 11 10  |
| 1        | 0 | O  | 1    | 1. | Ó   | 37<br>1 1) x   |
| 1        |   | 1  | 1    | ×  | 0 ( | R=KA) 1 Kanp   |
| 1        | 1 | 0  | 1    | 1  | D   | $\begin{array}{c ccccccccccccccccccccccccccccccccccc$  |
| T        | 1 | 1  | 0    | 0  | 1   | $\Rightarrow \qquad \qquad$ |

S=Jan R=Kan \_




Step5

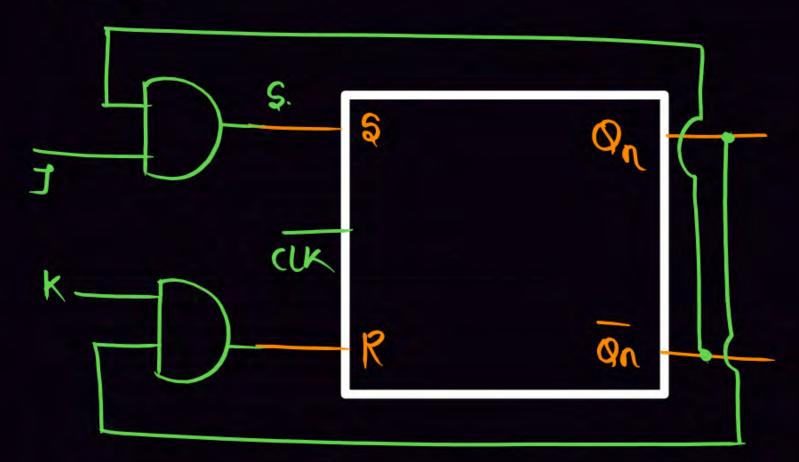


S=Jan R= Kan \_



Steps.

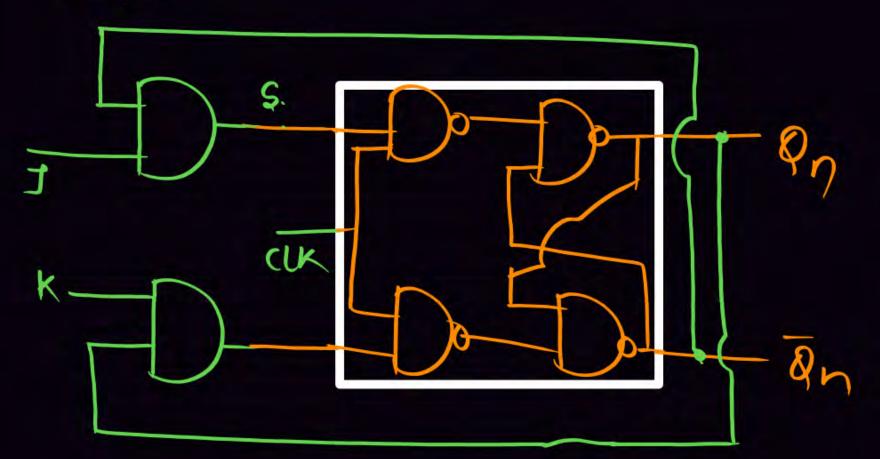



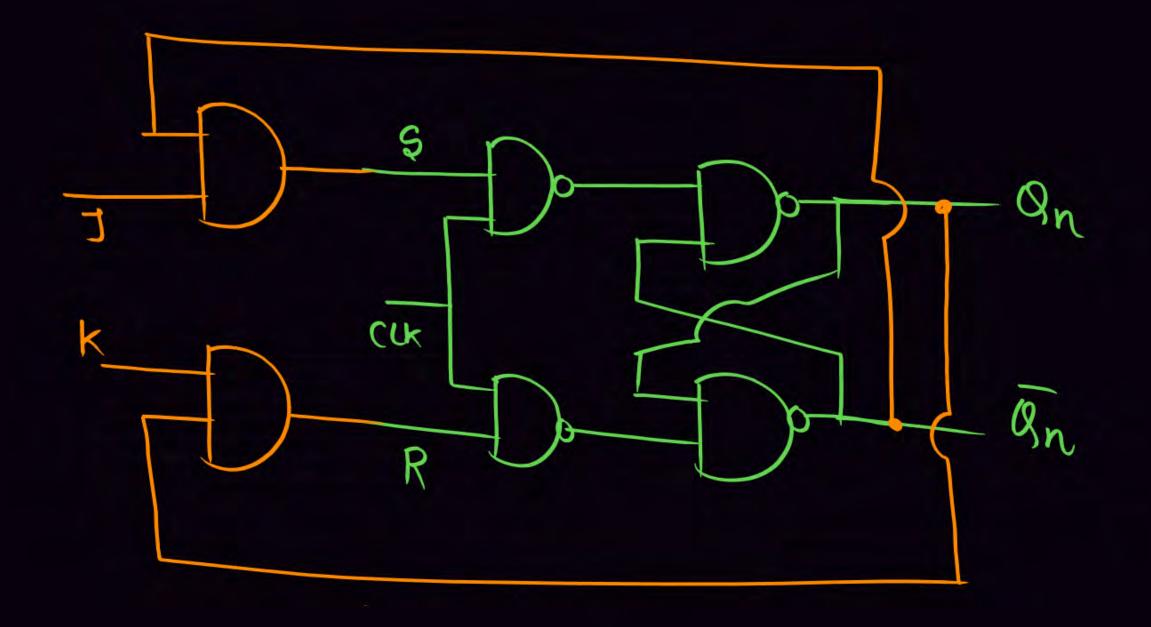



Q Resign a D-FF by using s.R. FF?




|   | Step 1: |
|---|---------|
| 1 | Step 2. |

|   | 9n | Onts | S | R |
|---|----|------|---|---|
| 0 | 0  | 0    | 0 | X |
| 0 | 1  | 0    | 0 | J |
| 1 | 0  | 1    | 1 | O |
| 1 | J  | J    |   | 0 |

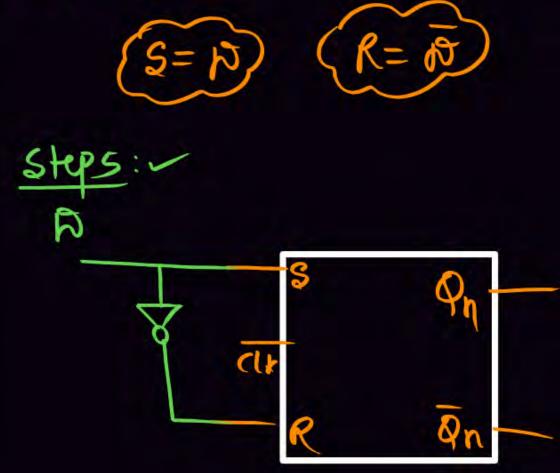

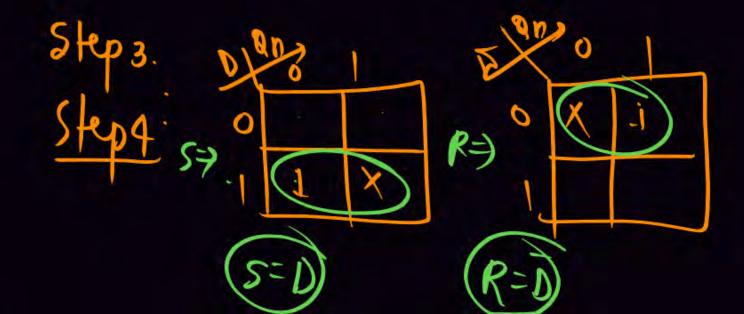



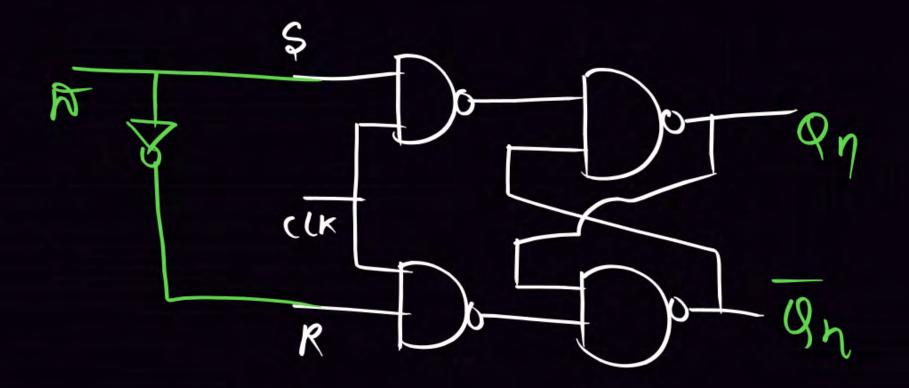


## a Resign a T-FF by using SRFF?



| 6 | ète | 7 | 1     |
|---|-----|---|-------|
| 6 | 5+  | 4 | المرا |


| T |   | Onti | Ş | R |
|---|---|------|---|---|
| 0 | 6 | 0    | 0 | X |
|   | 1 | 1    | X | 0 |
| 1 | O | 1    | 1 | 0 |
| L | 1 | 0    | 0 | 1 |

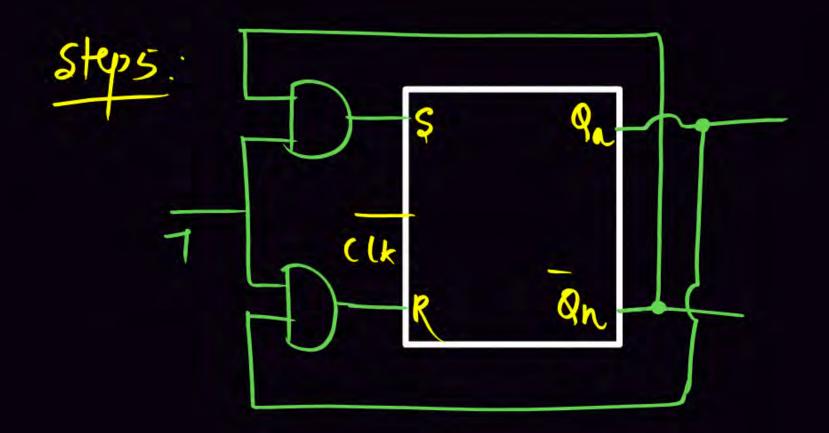


Pw W

## a Pesign a T-FF by Using P-FF?

| T |   | Qn+ | B |
|---|---|-----|---|
| 0 | 0 | 0   | 0 |
| 0 | ι | t.  | 1 |
| 1 | 0 | 1   | 1 |
| 1 | 1 | 0   | 0 |

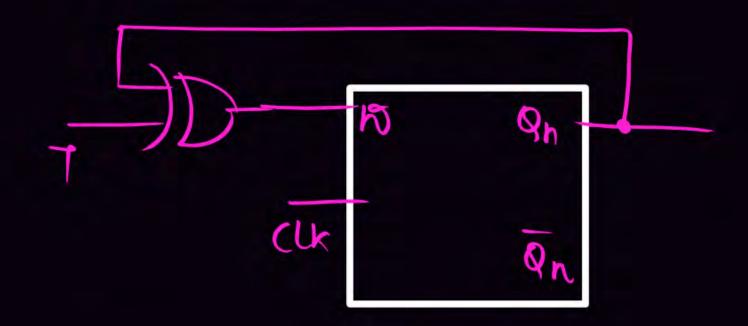



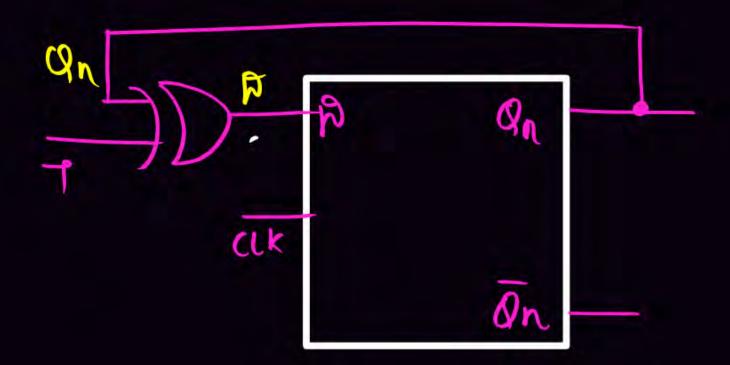


#### Method (1)

|   |    |      | PIF |
|---|----|------|-----|
| T | gu | gnt! |     |
| 0 | O  | 0    |     |
| Ò | 1  | 1    |     |
| 1 | 0  | 1    |     |
| L | 1  | 0    |     |

## a Design a R-FF by using 7-FF?



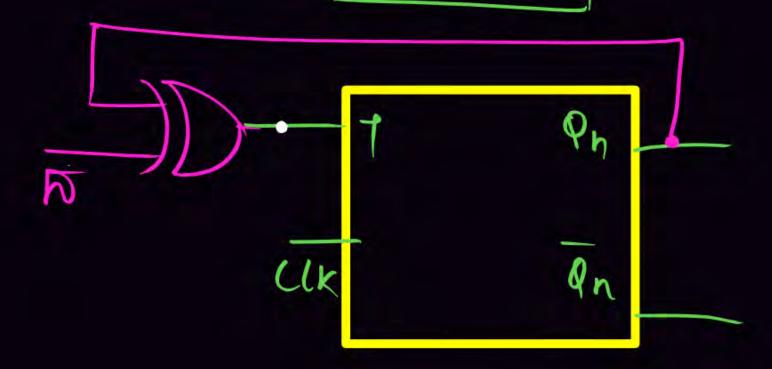

$$Q_{n+1} = T \oplus Q_n$$

$$T = D \oplus Q_n$$

$$Q_{n+1} = D \oplus Q_n \oplus Q_n$$

$$= D \oplus Q_n \oplus Q_n$$

$$= D \oplus Q_n$$



$$4 \times 3 = (12)$$
 $12$ 
 $5$ 
 $4$ 

Pw

## HIP Plesign a CJ FF by using T-FF?

| C | 7   | anti |
|---|-----|------|
| 0 | O   | On   |
| ď | 1   | an   |
| 1 | 0   | 0    |
| L | . 1 | 1    |



## Thank you

# Soldiers!

