CS & IT



ENGINERING

Digital Logic Logic GATE



Lecture No. 5



By- CHANDAN SIR



TOPICS TO BE COVERED 02 XNOR GATE

03 Questions Practice

04 Discussion



INVERTER

AND

OR

(770)

HAND

NOR





AB QI AB+(D A.R = AtB B

Pw

$$A \longrightarrow D \longrightarrow A \oplus B = \overline{A} B + A \overline{B}$$

$$= (\overline{A} + \overline{B}) (A + B)$$

$$A \oplus O = A$$

$$A \oplus \overline{A} = 1$$



$$A = A \oplus (A \oplus A)$$

$$A = A \oplus O$$

$$0 = 0 \cdot \Theta 0$$


$$A \oplus A \oplus A \cdots \oplus A = \begin{cases} O & \text{Even no. of } A \\ A & \text{odd no. of } A \end{cases}$$









Find the output y.

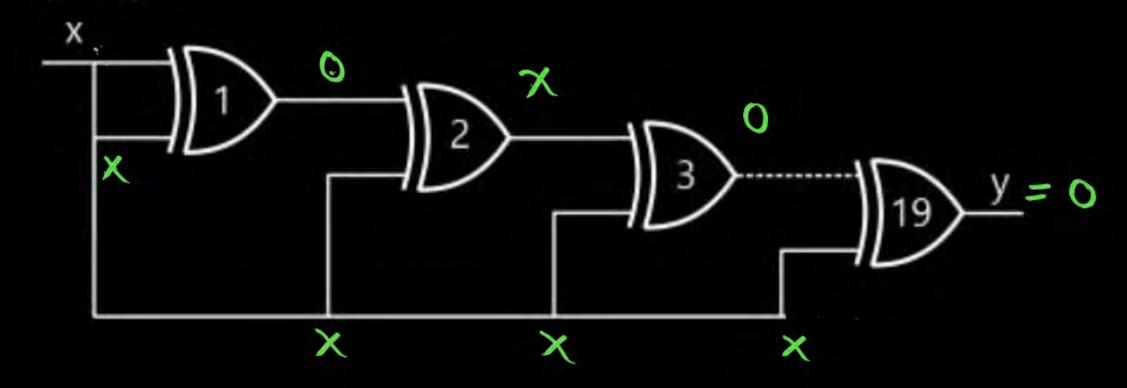


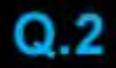



Find the output y.

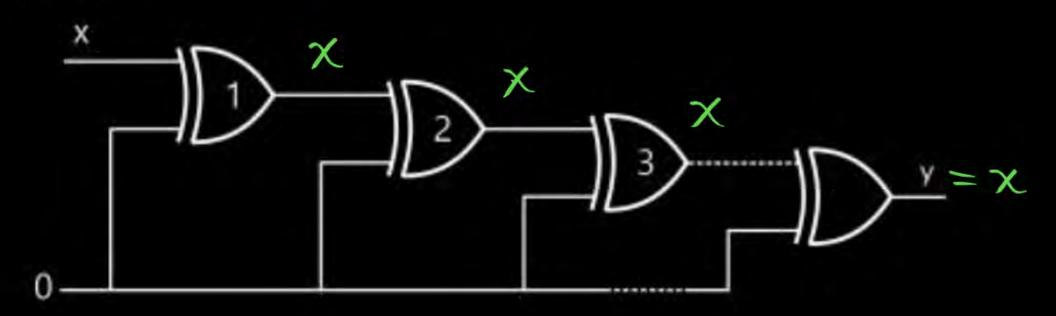


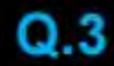

$$\begin{array}{r}
 \chi \oplus \bar{\chi} = 1 \\
 \chi \oplus 1 = \bar{\chi} \\
 \bar{\chi} \oplus 1 = \bar{\chi}
 \end{array}$$




Find the output y.

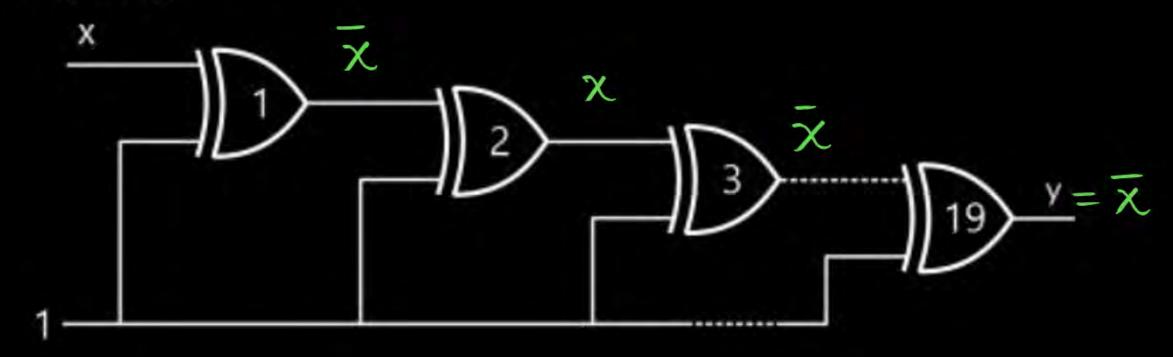

Symbol

Truth Table



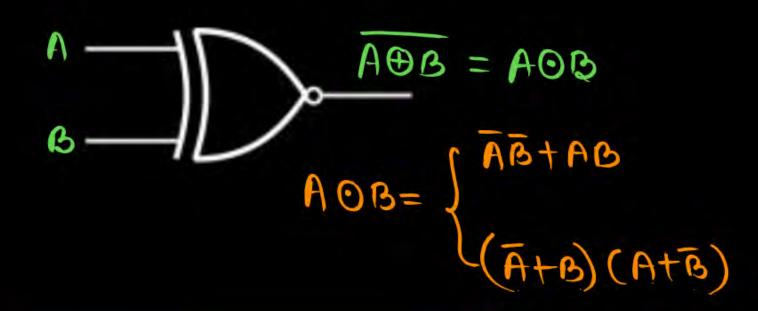

A	B	y = A ⊙ B
0	0	1
0	1	0
1	0	0
1	1	1

$$3 + A = B \qquad Y=1$$

$$A = \overline{G}$$
 $Y = 0$

A	В	y = A 🗿 B
0	0	1
0	1	0
1	0	0
1	1	1



$$A \odot A = 1$$

$$A \odot 1 = A$$

$$A = A \circ A$$

$$A = A \circ A$$

$$A = A \circ A$$



A	В	y = A 🗿 B
0	0	1
0	1	0
1	0	0
1	1	1



(<u>5</u>)

Olp=1 When Even no. of 15 are present in the input

Equal detector


or Equipalance Logic

Coincidance Logic

A	В	y = A 🗿 B	
0	0	1	
0	1	0	
1	0	0	
1	1	1	



6.

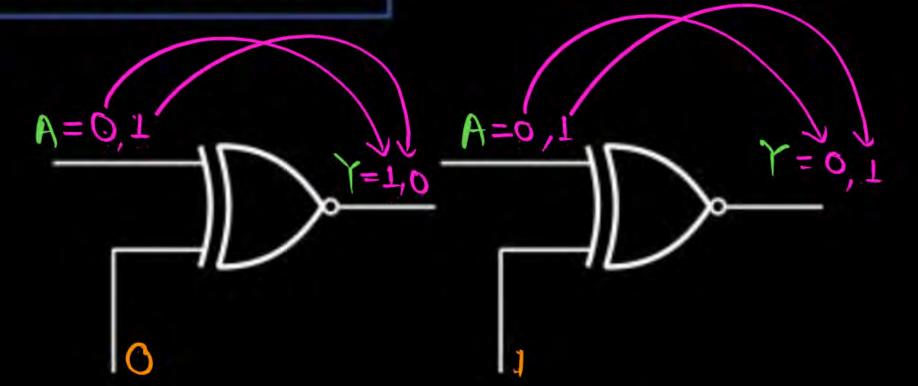

"INVERTER"

BUFFER

XOR GATE, X-NOR GATE



Commutative Law - follow karda hai.

$$A \odot B = B \odot A$$

X-NOR follows commutative as well as associative Law



X-NOR

Even no of input



Even Variable.

for Even input X-NOR GATE

number of 1's are present in the inputs.



Odd Variables in X-NOR GATE

of high when odd no of is in the inputs.






(AOB)O(= \(\int m(1,2,9,7) = A\(\operatorname{B}\(\operatorname{D}\(\operatorname{C}\)

Associate Law

	ABC	A O B O C	(A ⊙ B) ⊙ C
O >	000		0
1-	001		1
2→	010		1
3->	011		0
4->	100		1
5→	101		0
6→	110		0
7-1	111		1

For Odd Number of Input

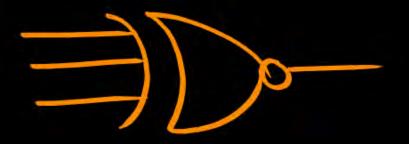

aisa practical nahi hai.



X-NOR

when Even no of I's are connected in the inputs.



olphigh
for even
no. of 1's
in the inputs.

=>DonDox-or 0/2 will be high

of will be high when odd no. of 1's in input.

Olp high when even no. of i's are connected in the inputs.



Alternate Symbol

$$\begin{array}{c}
A \oplus B = \overline{A} \circ \overline{B} \\
= \overline{A} B + A \overline{B} \\
= (\overline{A} + \overline{B})(A + B)
\end{array}$$



$$AOX$$

$$= \overline{A}\overline{X} + A\overline{B}$$

$$= \overline{A}\overline{B} + A\overline{B}$$

$$= \overline{A}B + A\overline{B}$$

$$= \overline{A}B + B$$

$$= \overline{A}B + B$$












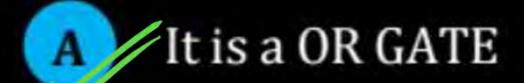The Boolean function given below: $f(A, B) = A \oplus B \oplus AB$ which statement is/are correct?





- B It is a NAND GATE
- It requires 3 NAND gate to implement the function
- It required 2 NAND gates to implement the function



AUB=X = ABTAB

ABB=X = AOB = FB+AB

$$\Rightarrow AB+AB+AB \Rightarrow A+AB = (A+A)(A+B) = A+B$$

$$\Rightarrow A(B+B)+AB \Rightarrow A+AB = (A+A)(A+B) = A+B$$




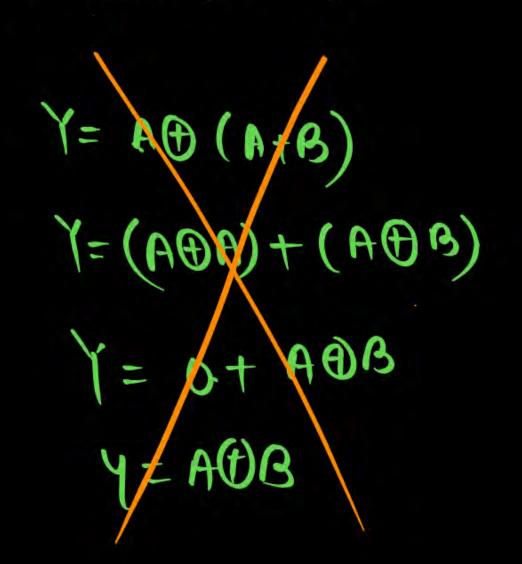Q.5



Minimized expression will be $Y = A \oplus (A + B)$

- $A \oplus B$
- **B** A ⊙ B
- **G** Ā⋅B
- D A + B



X-OR does not follow distribution Law over OR MATE.



$$Y = A\Theta (A+B) \qquad A+B = X$$

$$Y = A\Theta X$$


$$= \overline{A}X + A\overline{X}$$

$$= \overline{A} (A+B) + A (\overline{A+B})$$

$$= \overline{A} \cdot A + \overline{A} \cdot B + A \cdot \overline{A} \cdot \overline{B}$$

$$= O + \overline{A}B + O$$

$$= \overline{A}B$$

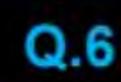








If the output y = 1
Then correct input is/are-

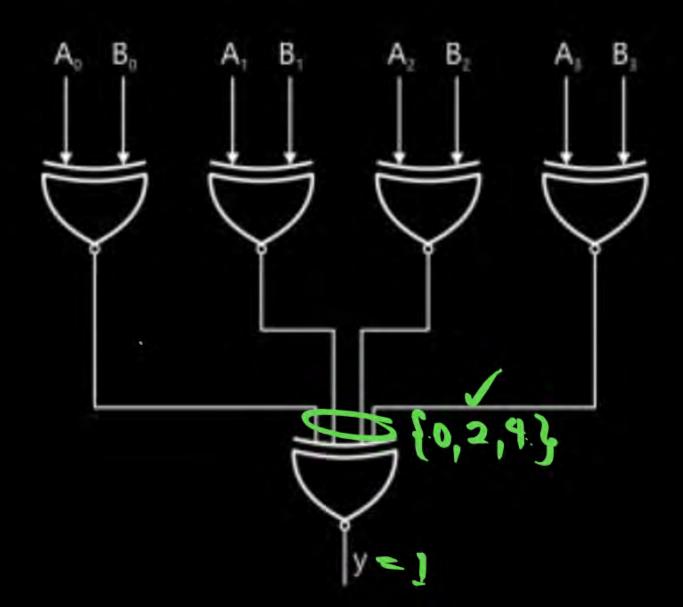- A 1111, 0000
- B 1010,0111×
- C 0101, 0101
- D 1100, 1110



Q.7

MCg

Output y will be-

$$Y = (PO\overline{P})O(\overline{Q}OQ)$$




1



 $A \oplus B$

$$A \oplus B \oplus C \oplus D$$

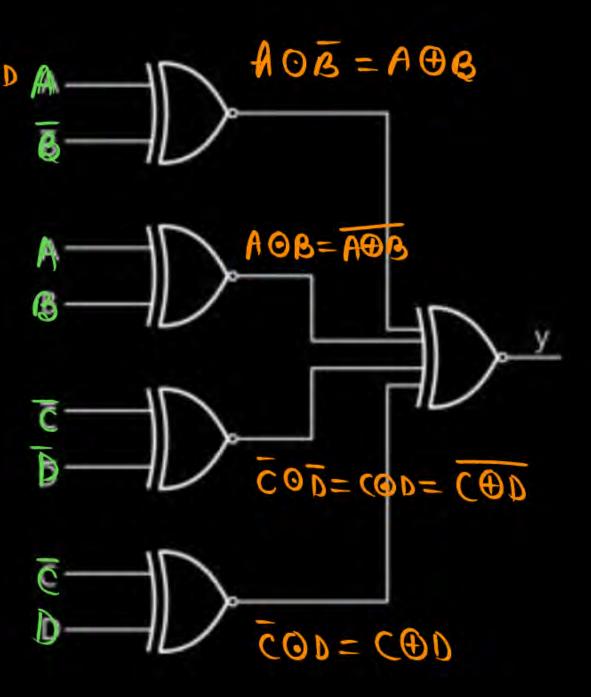



Which one of the following is NOT a valid identity?

[GATE-2019-CS: M]

$$A (x + y) \oplus z = x \oplus (y + z)$$

B
$$(x \oplus y) \oplus z = x \oplus (y \oplus z)$$

$$x \oplus y = x + y$$
, if $xy = 0$

D
$$x \oplus y = (xy + x'y')'$$

$$X\Theta Y = \overline{XY + XY}$$

$$= (\overline{X} + \overline{Y})(X + Y)$$



Given f1, f3 and f in canonical sum of products form (in decimal) for the circuit

GATE-2008-CS: 1M

 $\Sigma m (4,6)$

 $F_3 = \sum m (1, 6, 15)$

 $F = \sum m (1, 6, 8, 15)$

 $\sum m (4, 8)$

Then f2 is

 $\Sigma m (4, 6, 8) \neq$



Consider three 4-variable functions f1, f2 and f3, which are expressed in sum-ofminterms as

 $f_1 = \Sigma(0, 2, 5, 8, 14), f_2 = \Sigma(2, 3, 6, 8, 14, 15), f_3 = \Sigma(2, 7, 11, 14)$

For the following circuit with one AND gate and one XOR gate, the output

function f can be expressed as:

[GATE-2019-CS: M]

pressed as:
$$\{9,8,14\}$$
 [GATE-2019-CS: $\{2,3,6,8,14\}$ $\{3,4,14\}$ $\{3,4,14\}$ $\{3,4,14\}$ $\{4,6,6\}$ $\{4,6,14\}$ $\{4,6,6\}$ $\{4,6,14\}$ $\{4,6,6\}$ $\{4,6,14\}$ $\{4,6,6\}$ $\{4,6,14\}$ $\{4,6,6\}$ $\{4,6,14\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6,6\}$ $\{4,6\}$

- $\Sigma(2, 14)$
- Σ (7, 8, 11)
- Σ (2, 7, 8, 11, 14)
- Σ (0, 2, 3, 5, 6, 7, 8, 11, 14, 15)



Let ⊕ and ⊙ denote the Exclusive OR and Exclusive NOR operations, respectively. Which one of the following is NOT CORRECT?

[GATE-2018-CS: M]

$$\overline{P \oplus Q} = P \odot Q \checkmark$$

$$\bar{P} \oplus Q = P \odot Q \checkmark$$

$$\bar{P} \oplus \bar{Q} = P \oplus Q$$

$$P = \overline{P} \oplus \overline{P} \oplus Q = (P \odot \overline{P}) \odot \overline{Q}$$

$$1 \oplus \emptyset \qquad 0 \odot \overline{Q}$$


$$\overline{Q} + \overline{Q}$$



Consider the Boolean operator # with the following properties:

 $x\#0=x, x\#1=\bar{x}, x\#x=0 \text{ and } x\#\bar{x}=1$

Then x#y is equivalent to

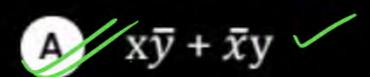

B
$$x\bar{y} + \bar{x}\bar{y}$$

$$\bar{x}y + xy$$

D
$$xy + \bar{x}\bar{y}$$

$$O = X \oplus X$$

$$\times \oplus 0 = \times$$

$$|=\bar{\chi} \oplus \chi$$

MCQ HW



Let, $x_1 \oplus x_2 \oplus x_3 \oplus x_4 = 0$ where x_1 , x_2 , x_3 , x_4 are Boolean variables, and \oplus is the XOR operator.

Which one of the following must always be TRUE?

[GATE-2016-CS: M]

- $A \quad x_1 x_2 x_3 x_4 = 0$
- B $x_1x_3 + x_2 = 0$
- $\overline{x_1} \oplus \overline{x_3} = \overline{x_2} \oplus \overline{x_4}$

MCQ HW



The binary operator ≠ is defined by the following truth table

P	Q	p≠q
0	0	0
0	1	1
1	0	1
1	1	0

Which one of the following is true about the binary operator ≠?

- Both commutative and associative [GATE-2015-CS: M]
- B Commutative but not associative
- Not commutative but associative
- Neither commutative nor associative

MCQ HW



Let \oplus denote the Exclusive OR (XOR) operation. Let T' and 'o' denote the binary constants. Consider the following Boolean expression for F over two variables P and Q:

$$F(P,Q) = ((1 \oplus P) \oplus (P \oplus Q)) \oplus ((P \oplus Q) \oplus (Q \oplus 0))$$

The equivalent expression for F is

[GATE-2014-CS: M]

- A P+Q
- B (P+Q)'
- $P \oplus Q$
- $P \oplus Q)'$



Which one of the following expressions does NOT represent exclusive NOR of x and y?

[GATE-2013] CS: M]

$$A \quad xy + x'y' = x0$$

B
$$x \oplus y' = \chi \otimes y$$


$$D/x' \oplus y' = X \oplus Y$$

MCQ HD



Which one of the following circuits is NOT equivalent to a 2-input XNOR (exclusive NOR) gate?

[GATE-2011-CS: M]

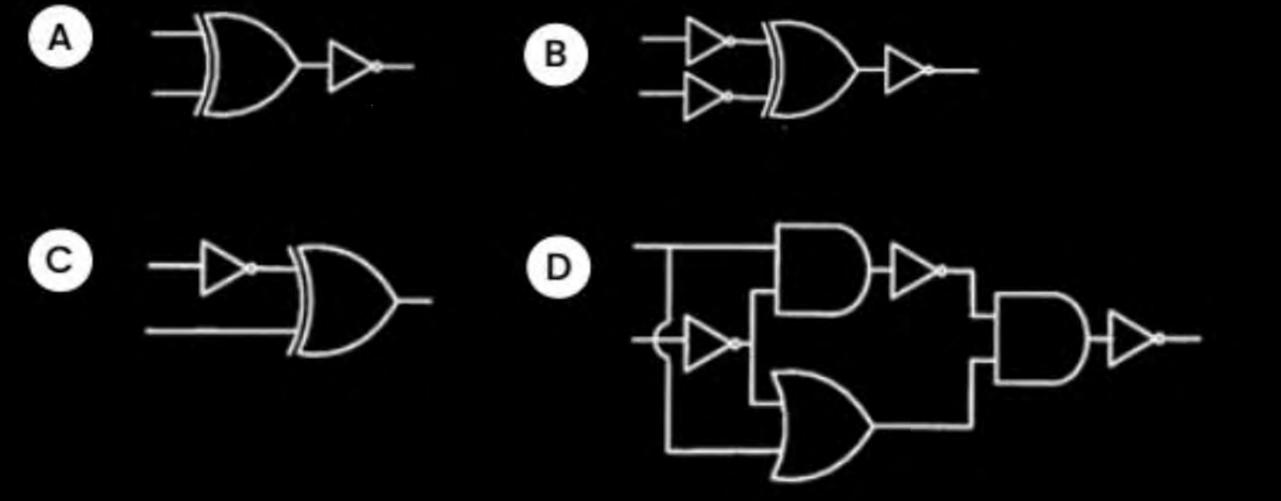



Thank you

Seldiers!

