# CS & IT



# ENGINEERING



Sequential Circuit

Lecture No. 2



By- CHANDAN SIR





TOPICS TO BE COVERED 01 SR & JK Flip Flop

**02** PRACTICE

**03** DISCUSSION



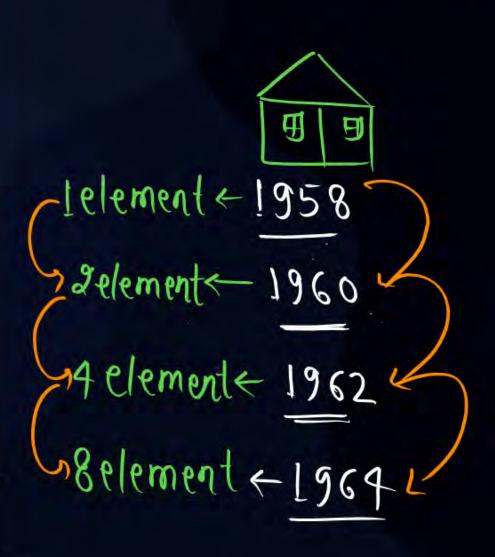


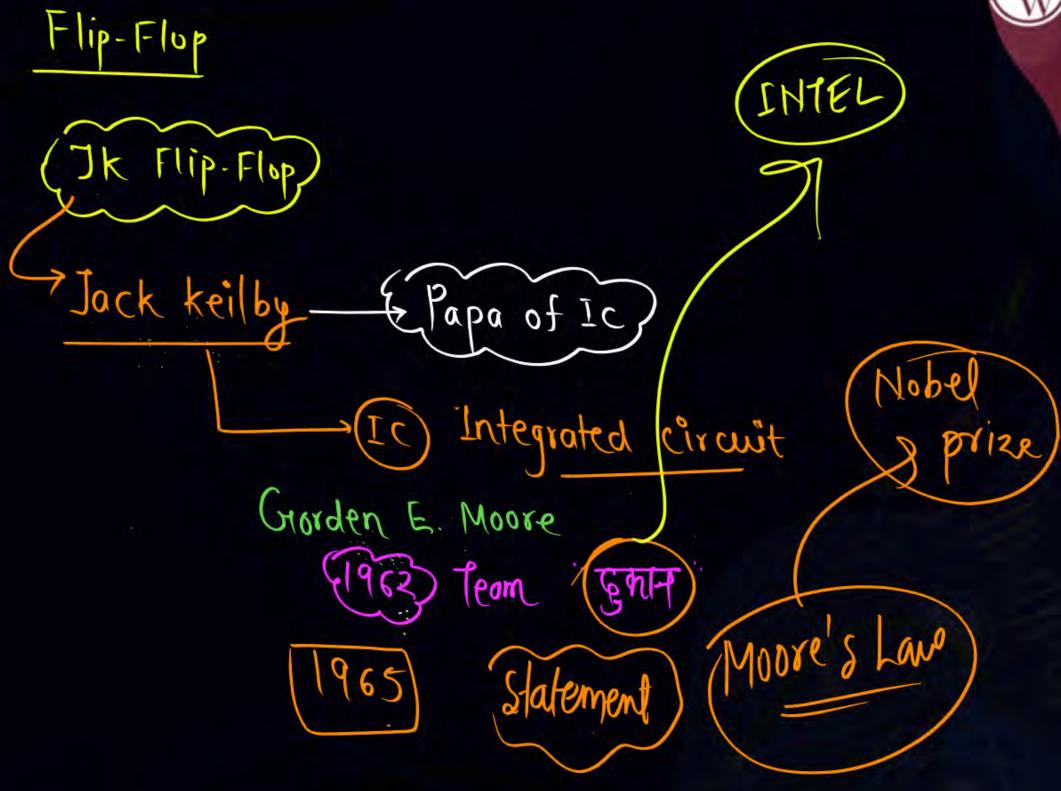



SR (Flip-Flop)

Flip-Flop.

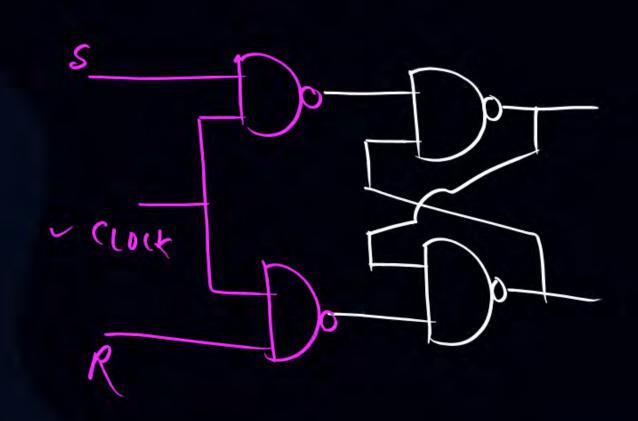






Crock




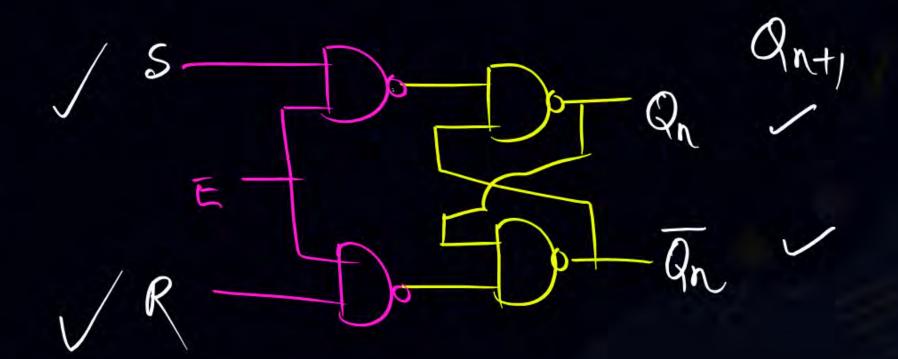
- De Circuit Diagram [symbol]
- 2 Truth table
- 3 Characteristic Table
- 1 Characteristic Equation
- (5) Excitation Table
- 6) State Riagram






### Circuit Diagram

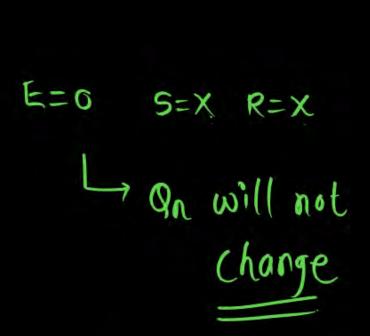

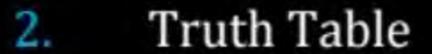

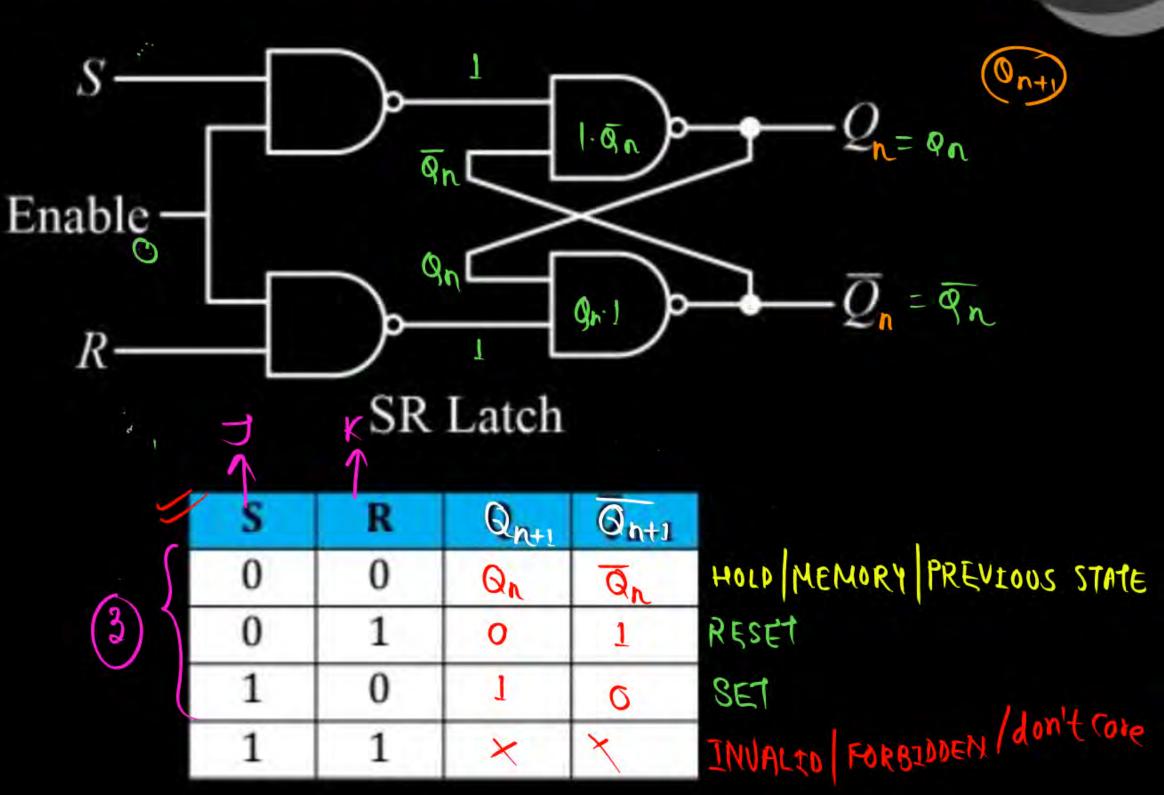





#### 3. Characteristics Table

	S	R	Qn	Q <sub>n+1</sub>
0	0	0	<b>Q</b> <sub>n</sub>	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1 -
5	1	0	1	1
6	1	1	0	×
7	1	1	1	×



### 4. Characteristics Equation

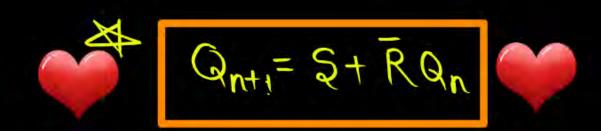

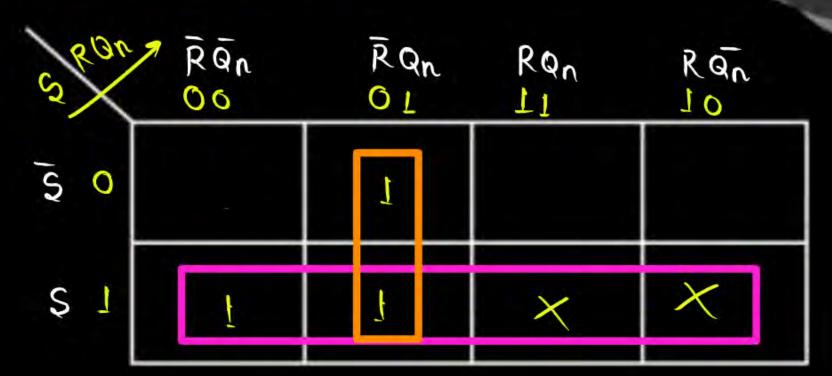




### Excitation Table


Qn	$Q_{n+1}$	S	R
0	0	0	X
0	. 1	1	O
1	0	0	1
1	1	X	0

_				9	
	Naya	(tex)	SHIC	Tab	P
		C. C.		( uc p	


S	R	Qn	Q <sub>n+1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	4
1	0	1	J
1	1	0	X
1	1	1	*


State Diagram

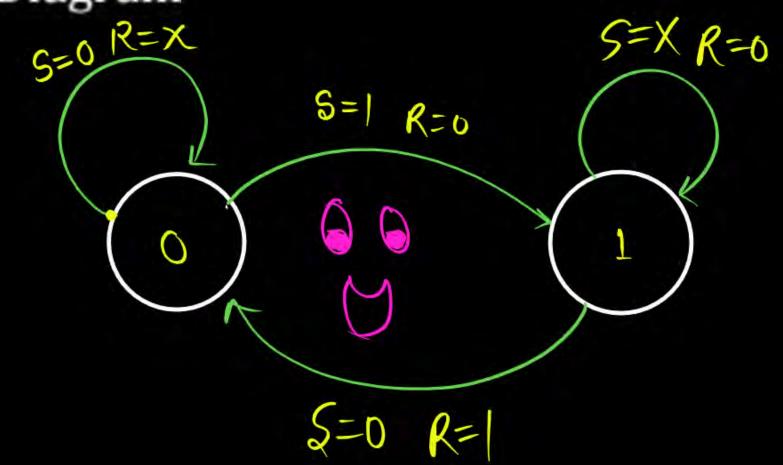

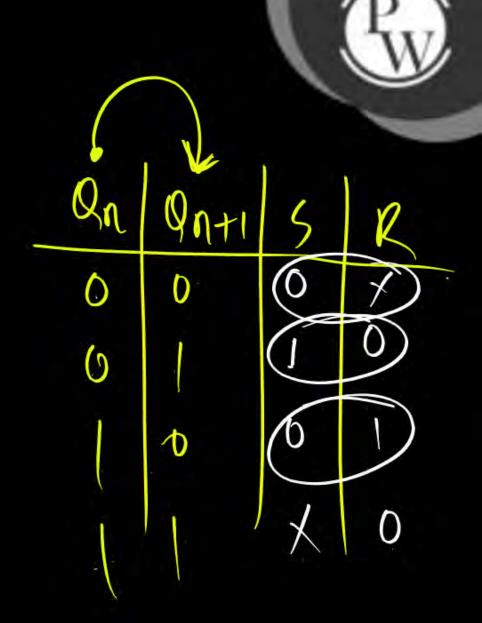

Symbol

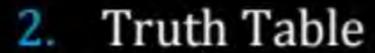

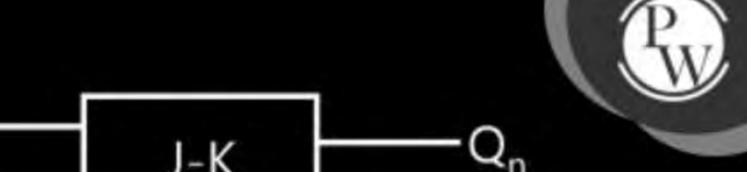



J	K	$Q_{n+1}$
0	0	Qn
0	1	0
1	0	1
.1	J	On



3. Characteristics Table




J	K	Qn	Q <sub>n+1</sub>
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



4. Characteristics Equation

1			

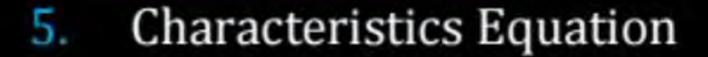

Q <sub>n</sub>	$Q_{n+1}$	J	K





# Thank you

Seldiers!

